

20 juni 2017  
1931 Congrescentrum Den Bosch

**POWER  
ELECTRONICS**

**2017**



# DC/DC Converters for IGBT, SiC, GaN and other Gate Drivers

Florian Boess, Business Development Manager, RECOM Electronic GmbH & Co. KG  
on behalf of Rutronik Netherlands, 20. June 2017

## RECOM Electronic main facts:


- Since 43 years on the market with DC/DC-Converters
- More than 30.000 products available in a huge partner network
- Own development and production in 3 fabs in Taiwan and China
- Isolated DC/DC-Converters from 0,25W up to 240Watt
- R-78 non isolated Switching regulator series up to 5A Iout
- AC/DC-Power Supplies from 1W up to 480W (Din Rail)
- New own EMC Lab for testing, special seminars and customers
- 3 to 7 years warrenty for the products
- Fully certified and qualified towards UL, EN, CE, ENEC etc.
- Industrial, Medical, new Energy, IoT / Sensors, Lighting, Railway etc.

# Introduction

- **Typical High Speed / High Power Switching Applications**
- **IGBT Construction and Gate Drive**
- **SiC Construction and Gate Drive**
- **Choosing the right DC/DC converter**
- **Other Drivers / GaN Technology**
- **Summary**

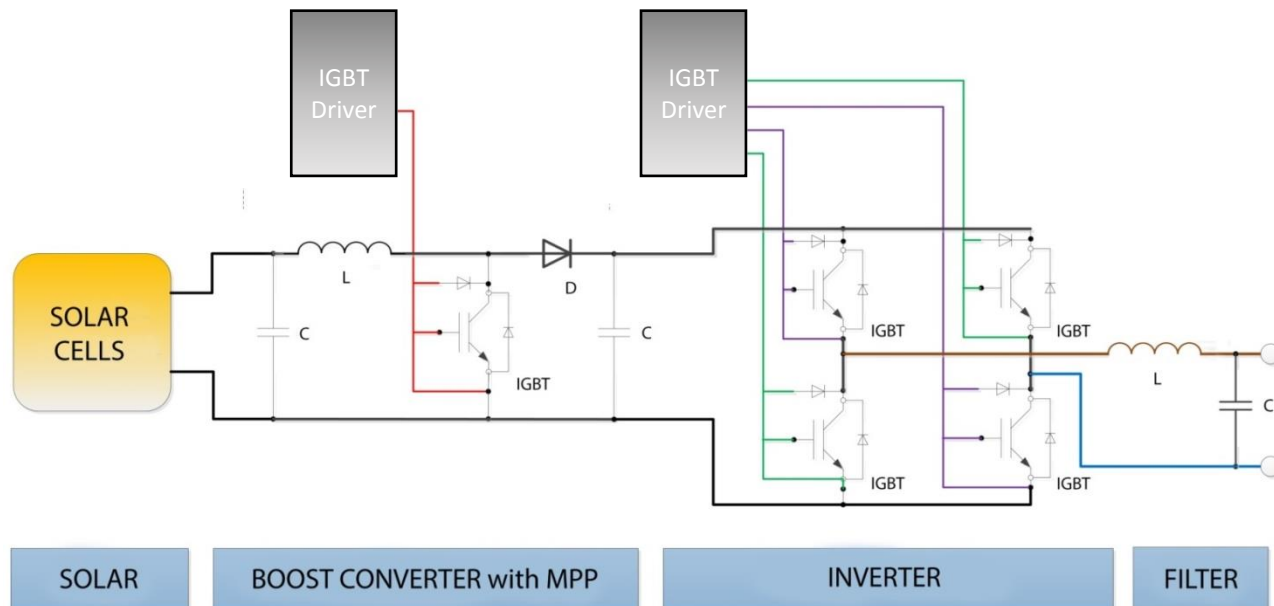
# Introduction

- Typical High Speed / High Power Switching Applications: Solar Inverter


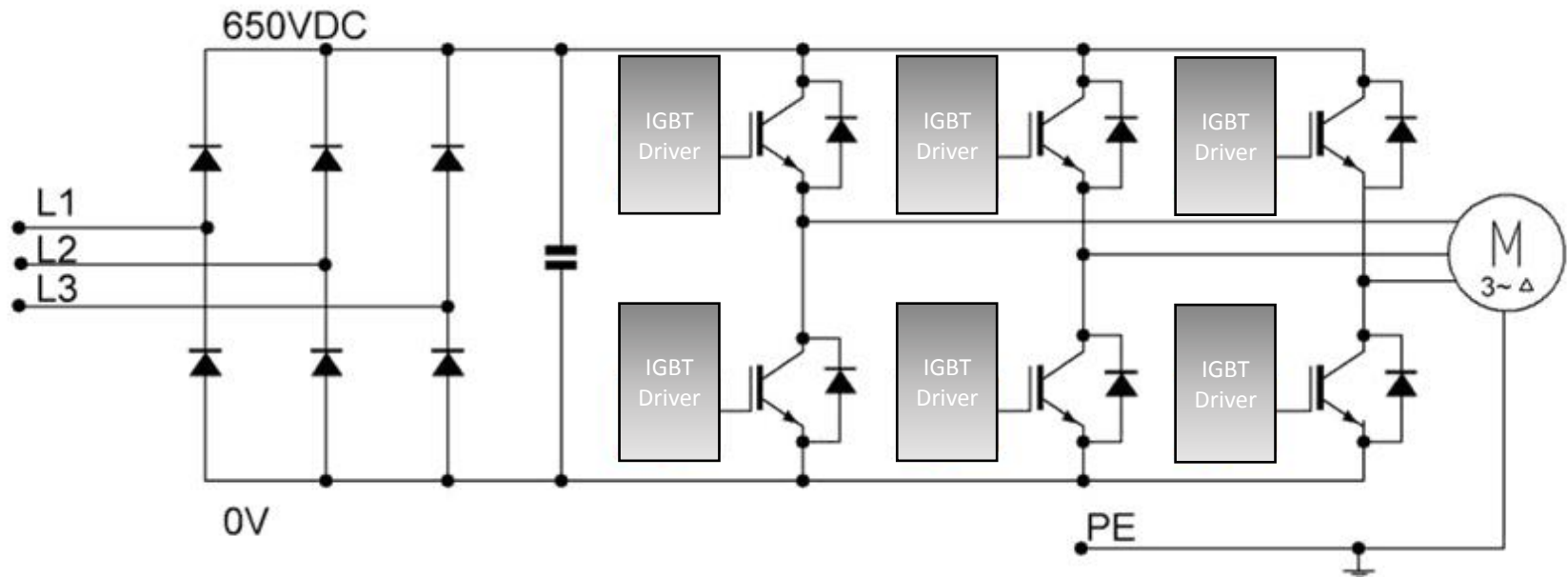
# Introduction


- Typical High Speed / High Power Switching Applications: Motor Controller




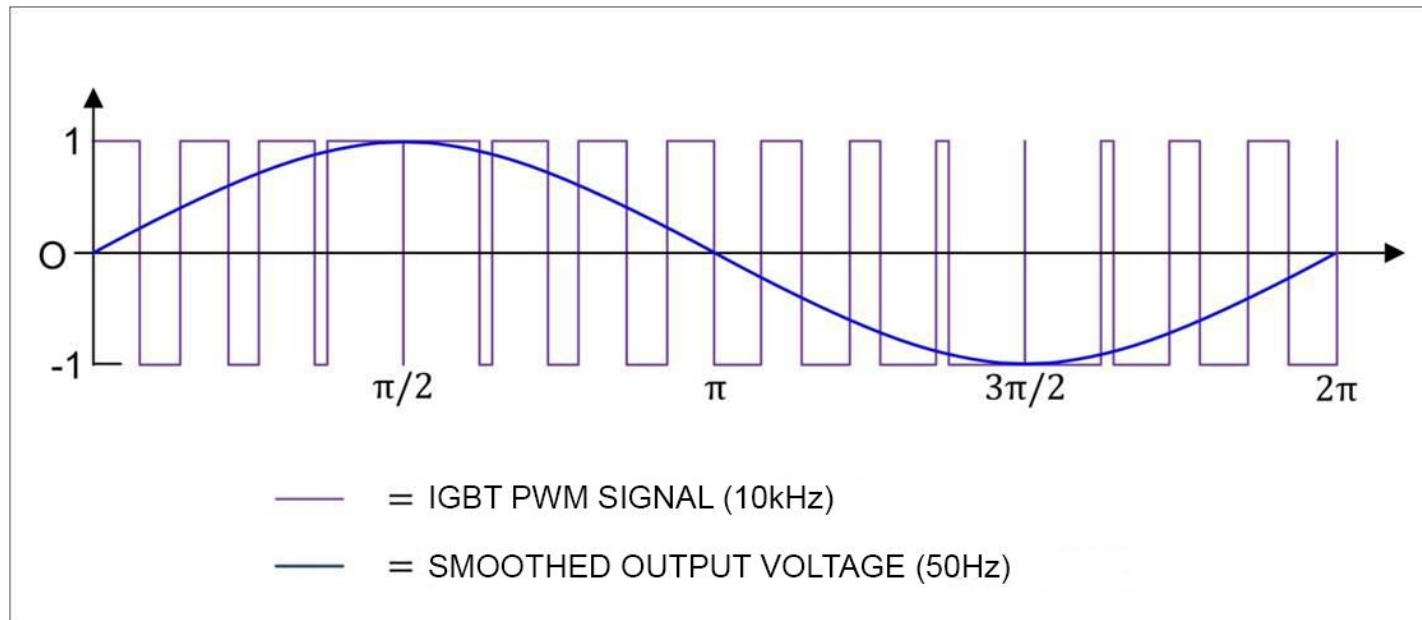
# Introduction

- **Typical High Speed / High Power Switching Applications: PWM Power control**




# Introduction

- **Typical High Speed / High Power Switching Applications: Typical Requirements**
  - High Voltage and Current
  - Fast turn on
  - Fast turn off
  - Reliable switching
  - Keep  $di/dt$  in check
  - Keep  $dv/dt$  in check

# Introduction to IGBT and SiC


## IGBT Construction

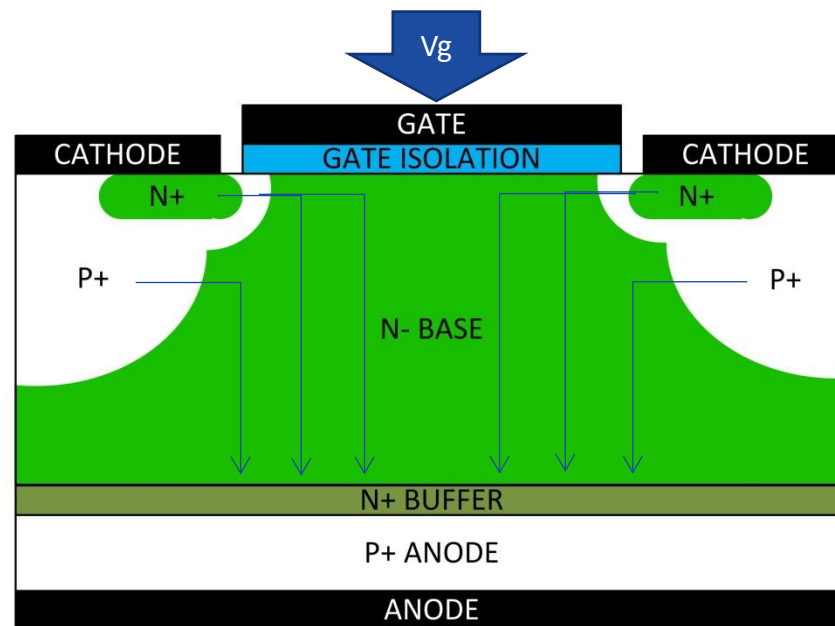




# Introduction to IGBT and SiC

## Turn On Gate Drive: IGBT

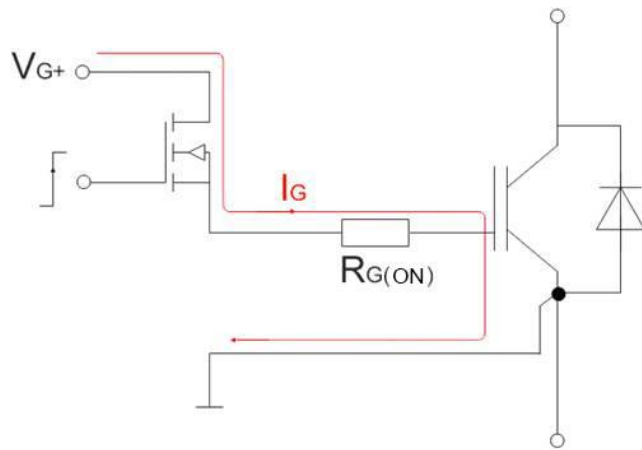


Gate Current at Turn ON

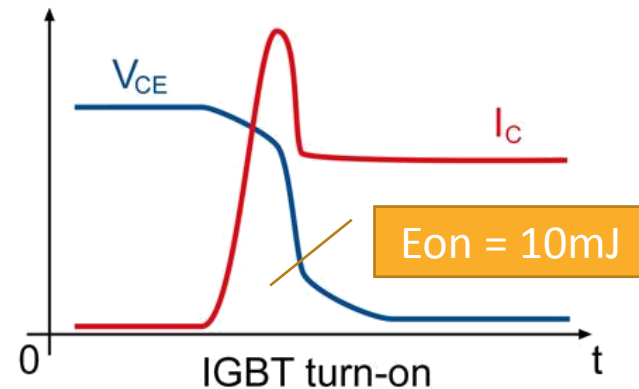

- Switching behaviour determined by gate capacitance
- Threshold +3V approx, but +15 needed for reliability
- Switching speed determined by gate resistor  $R_{G(ON)}$  and  $V_{G+}$  Voltage



# Introduction to IGBT and SiC

## IGBT Construction

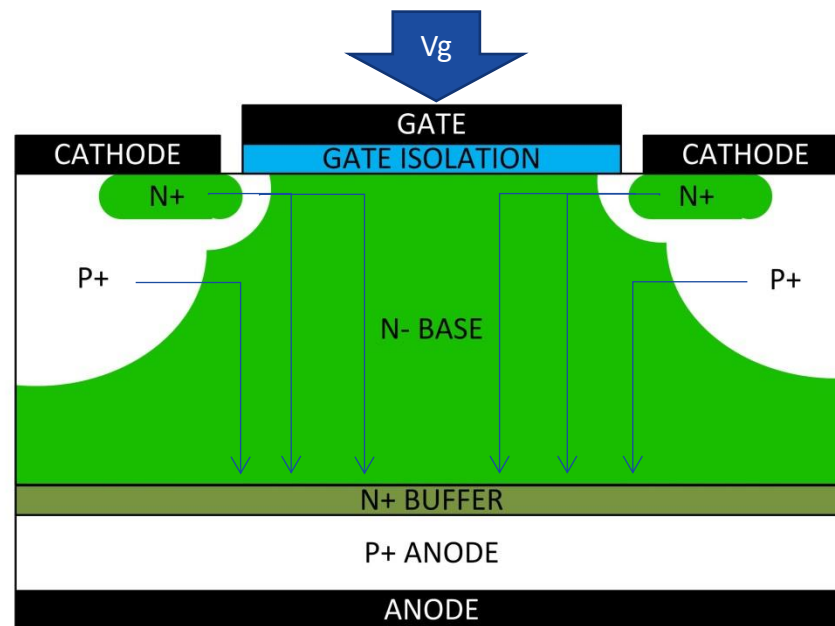

# Introduction to IGBT and SiC


## Turn Off Gate Drive: IGBT

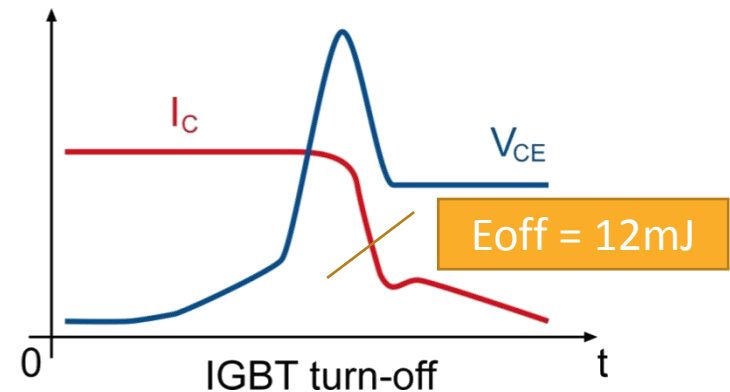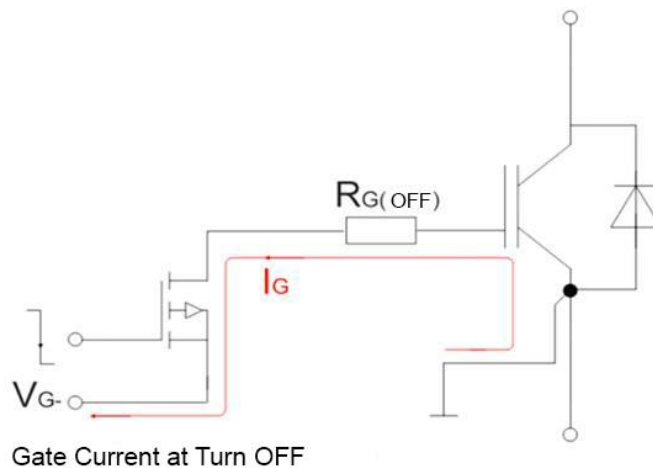

- Long tail-off (due to recombination time)
- Threshold +3V approx, but -9V needed for speed
- Switching speed determined by gate resistor  $R_{G(ON)}$  and  $V_{G-}$  Voltage

# Introduction to IGBT and SiC


## SiC Construction

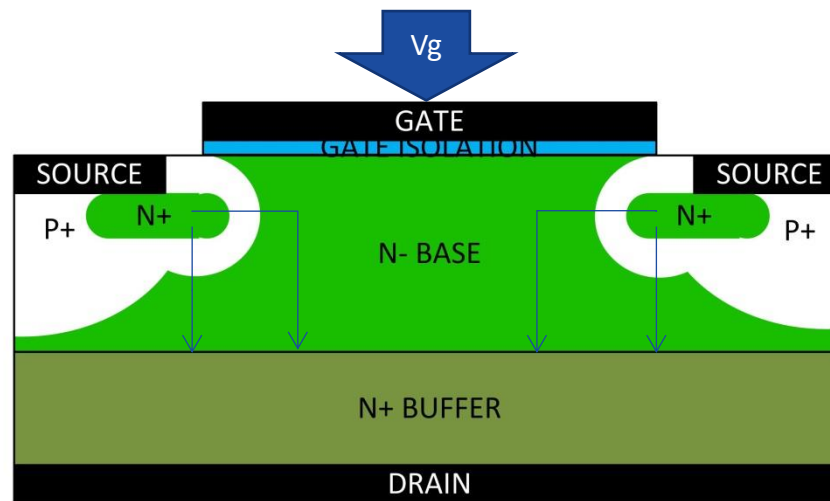


- 10x higher dielectric breakdown than Si (thinner layers = lower resistance)
- 3x better thermal conductivity (higher power rating)

# Introduction to IGBT and SiC

## Turn On Gate Drive: SiC

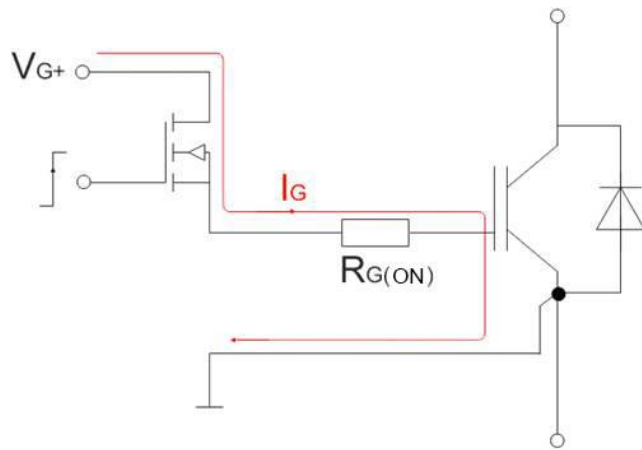


Gate Current at Turn ON

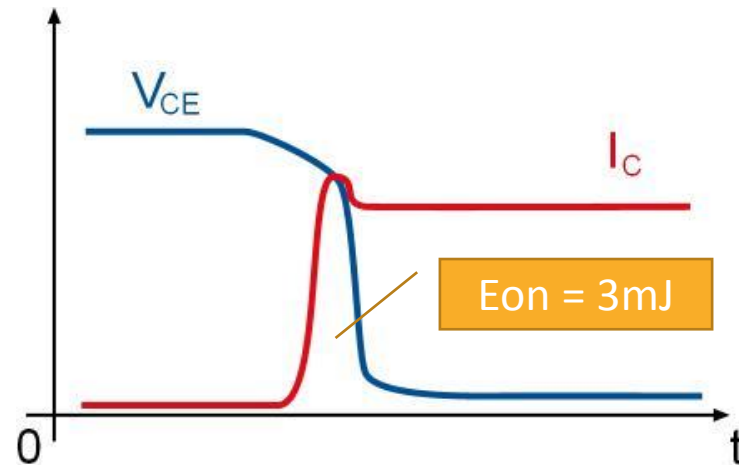

- Significantly lower switching dissipation
- No threshold voltage, but 18-20V needed to switch higher currents
- Switching speed mainly determined by gate resistor  $R_{G(ON)}$



# Introduction to IGBT and SiC

## SiC Construction

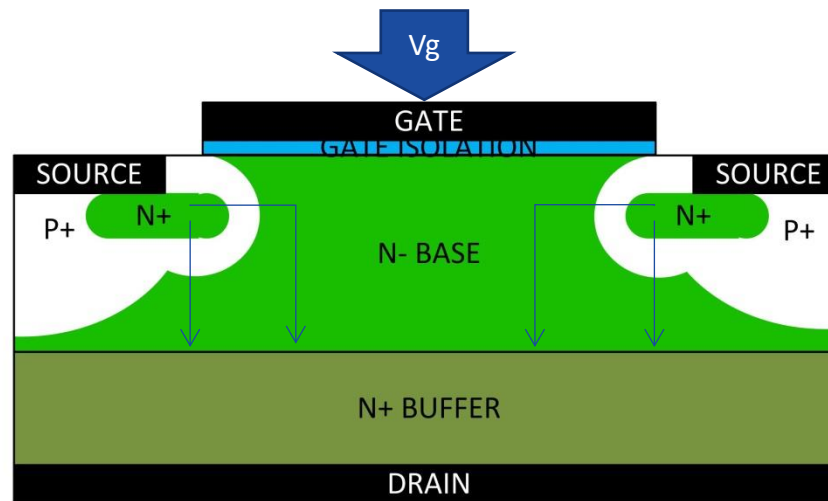

# Introduction to IGBT and SiC

## Turn Off Gate Drive

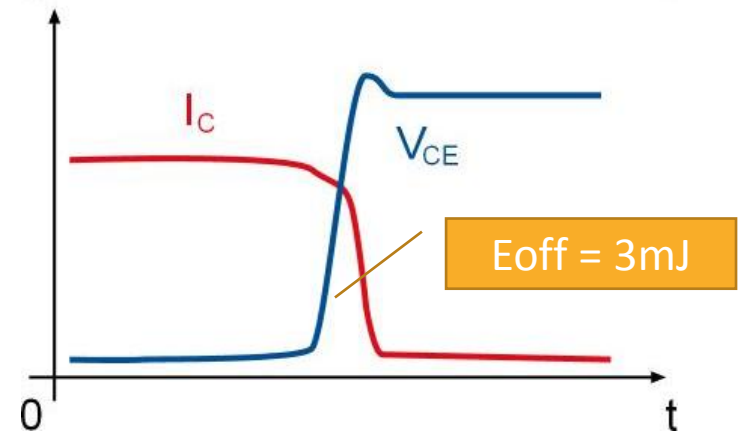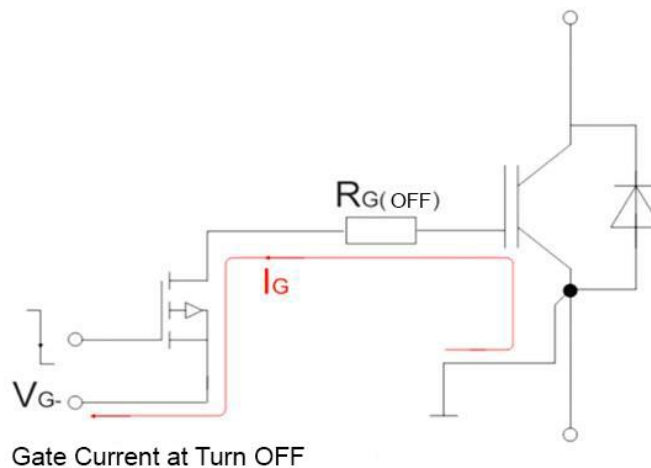


- On and Off switching behaviour very similar (no tail current)
- Threshold 0V, but -5V needed for reliability
- Switching speed mainly determined by gate resistor  $R_{G(OFF)}$

# Introduction to IGBT and SiC
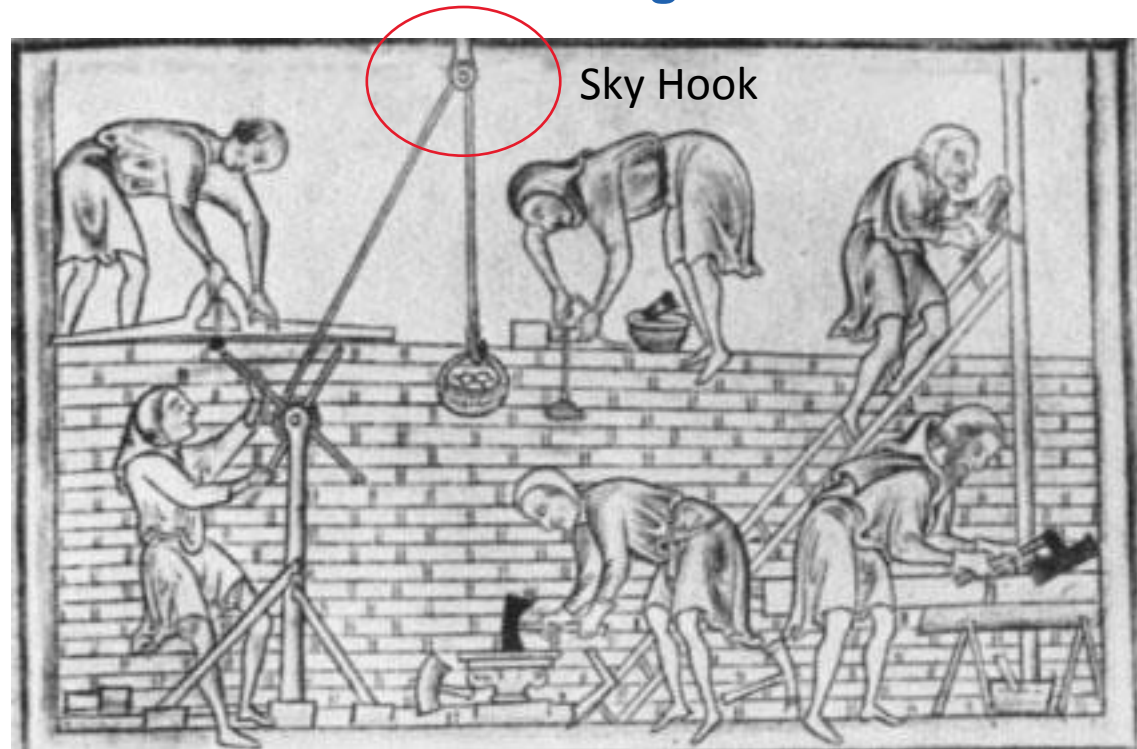
## Gate Driver - Where do these voltages come from?


In Mediaeval times, illustrators often drew in a „skyhook“ rather than explain how things were supported. The same with some IC manufacturers today!




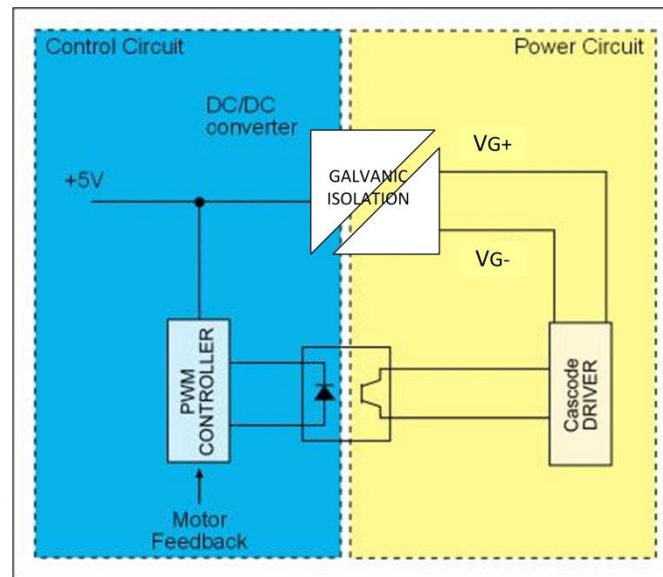
# Introduction to IGBT and SiC


An isolated DC/DC converter is needed to power the gate driver (electronic skyhook):



# Choosing the right DC/DC converter

## IGBT Gate Driver

Very little power is needed:

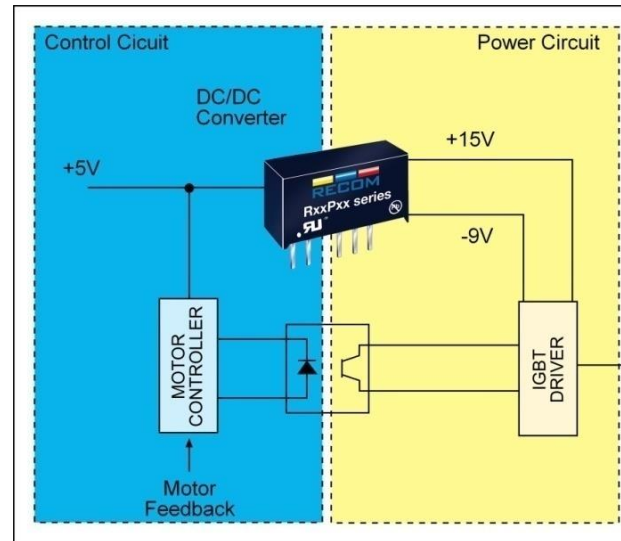


$$P_{gate} = P_{driver} + \left( Q_{gate} f_{sw} \Delta V_{gate} \right) + \left( C_{ge} f_{sw} \Delta V_{gate}^2 \right)$$

$$P_{gate} = 0.5W + 0.4W + 0.1W = 1W \quad (\text{for } 10\text{kHz})$$

# Choosing the right DC/DC converter

## SiC Gate Driver

Very little power is needed:

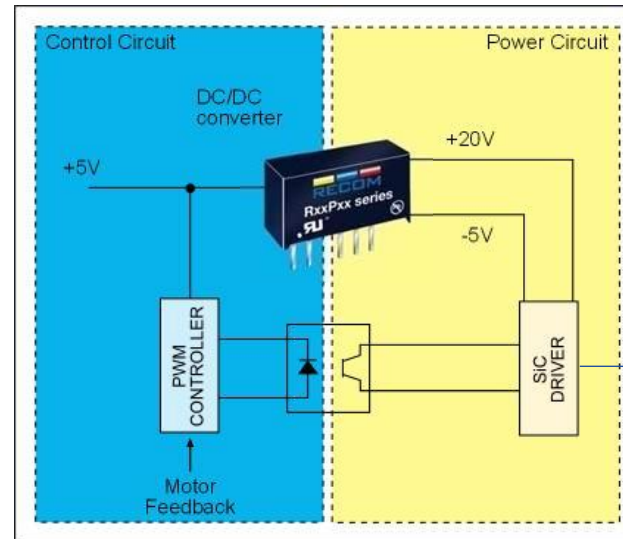

$$P_{gate} = P_{driver} + \left( Q_{gate} f_{sw} \Delta V_{gate} \right) + \left( C_{ge} f_{sw} \Delta V_{gate}^2 \right)$$


$$P_{gate} = 0.6 + 0.05 + 0.05 = 0.7W \quad (\text{for } 10\text{kHz}) \text{ e.g. RxxP2005D, } 1W$$

$$P_{gate} = 0.8 + 0.25 + 0.25 = 1.9W \quad (\text{for } 50\text{kHz}) \text{ e.g. RxxP22005D, } 2W$$

# Choosing the right DC/DC converter
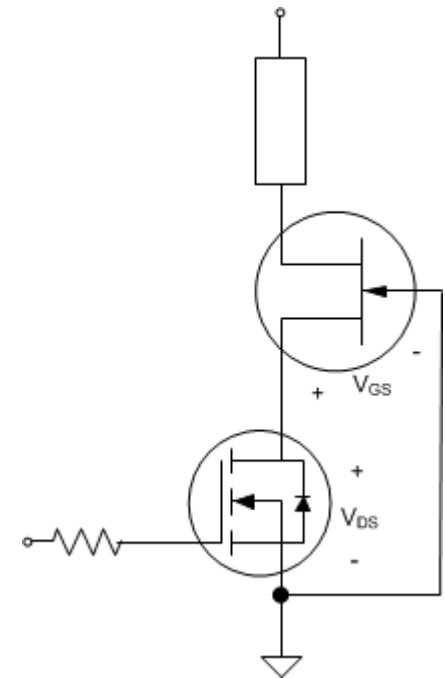
## Other Drivers- SiC/IGBT Cascode

- 30V IGBT controls a 1.2kV SiC JFET
- Threshold voltage around 5V
- Vgs drive = +15V / 0V (single-sided driver)
- Add JFET gate resistor to control di/dt




# Choosing the right DC/DC converter

## Other Drivers – SiC/IGBT Cascode

$$P_{gate} = P_{driver} + (Q_{gate} f_{sw} \Delta V_{gate})$$


$$P_{gate} = 0.6W + 0.1W = 0.7W \text{ (for 100kHz)}$$

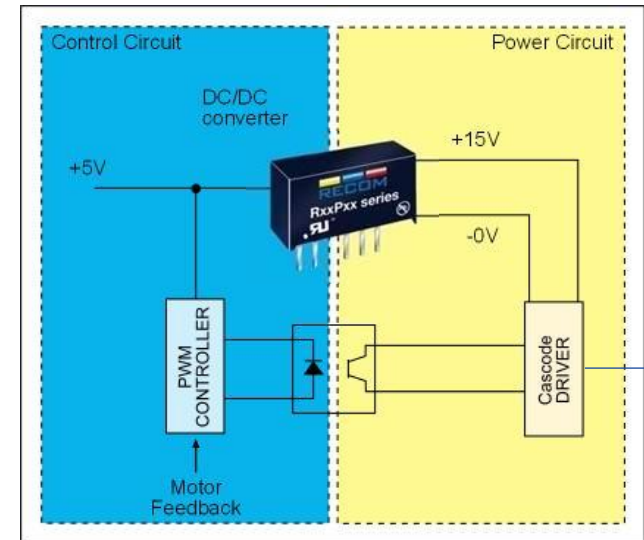- Low Power
- High Isolation
- e.g. R05P15S, 1W, 6.4kVDC Isolation



# Choosing the right DC/DC converter

## Other Drivers – Normally off GaN HEMT

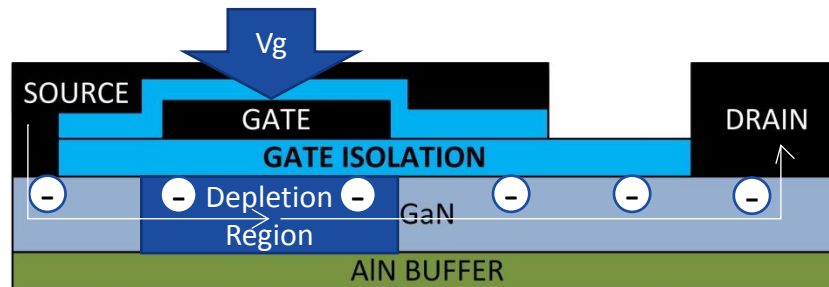

- Significantly lower switching dissipation (electron injection)
- Low threshold voltage (typically 1.4V) – Absolute max allowed  $V_{gate}=6V$
- Can be driven with single sided 5V driver


# Choosing the right DC/DC converter

## Other Drivers – Normally off GaN HEMT

$$P_{gate} = P_{driver} + (Q_{gate} f_{sw} \Delta V_{gate})$$

$$P_{gate} = 0.05W + 0.05W = 0.1W \quad (\text{for } 1\text{MHz})$$

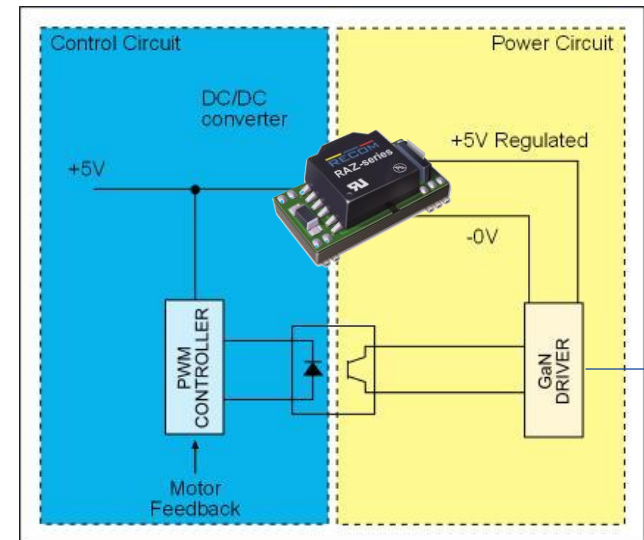
- Low Power
- Regulated output
- High Isolation
- e.g. RAZ-0505S, Regulated 1W, 2kVDC


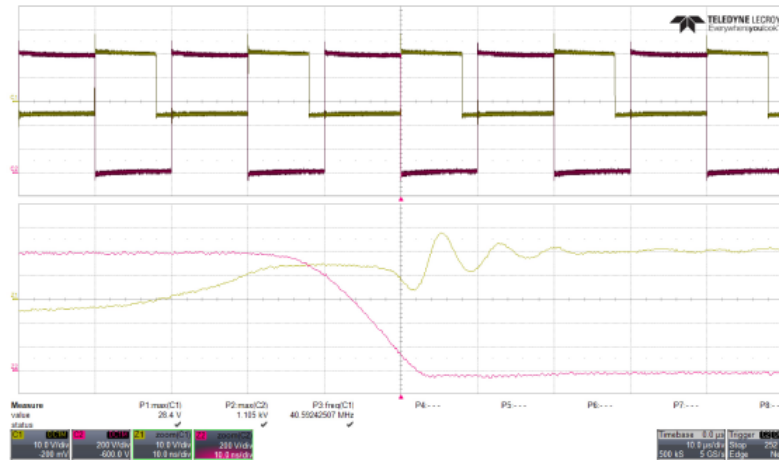
# Eval Board Example: 10kW: 100kV/ $\mu$ s slew rate, 50kHz



Lab Notebook Entry from LeCroy DSO  
DSO S/N: LCRY2807N56346  
User: LeCroyUser  
Time: 3/20/2017 3:35:40 PM




### Channel Status

	C1	C2	C3	C4
V/Div	10.0 V	200 V	10.0 V	500 mV
Offset	-200 mV	-600.0 V	-30.00 V	0 mV
Vertical	Coupling DC1M $\Omega$	DC1M $\Omega$	DC1M $\Omega$	DC50 $\Omega$
	BW-Limit 1GHZ	1GHZ	1GHZ	1GHZ
	Probe 10	100	1.000000	1.000000
	Sweeps 1#	1#	1#	1#

### Acquisition Status

Horizontal	Time / Div	10.0 $\mu$ s	Sampling Rate	5.000000000 GS/s
	Time / Pt	200.000 ps	Sampling Mode	RealTime
	Pts / Div	50.0000 kS	Trigger Delay	0.0 $\mu$ s
	Mode	Stop	Slope	Negative
Trigger	Type	Edge	Level	252 V
	Source	C2	Coupling	DC

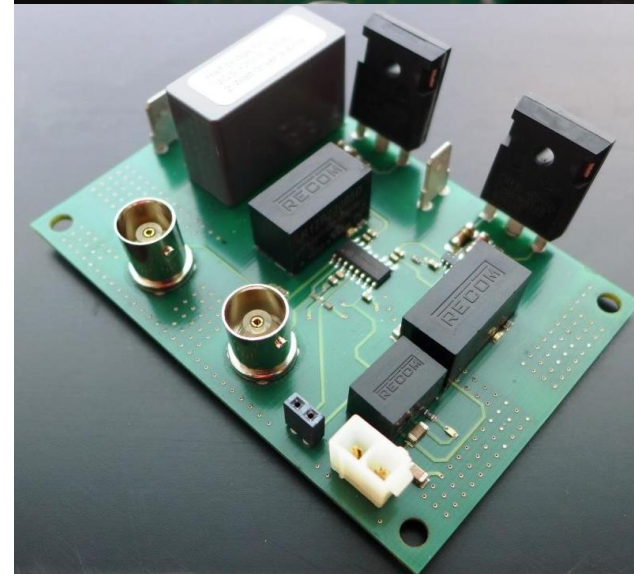



# Choosing the right DC/DC converter

## Examples for IGBT / SiC / GaN converters

### **High Isolated DC/DC for Medical and Industrial:**

**RxxPxx, RxxP2xx, RV, REC3.5, REC6, REM1, REM3, REM6, REM10**


- 1W and 2W in SIP7 package / 3W-10W in DIP24
- Reinforced Isolation construction up to 10kVDC
- REM: 2 MOPP for patient safety 250VACrms, 5kVAC/1min
- REM: Creepage and Clearance  $\geq$  8mm
- UL60601-1 3<sup>rd</sup> Ed. Medical approved



### **High Isolated DC/DC for IGBT/SiC/GaN:**

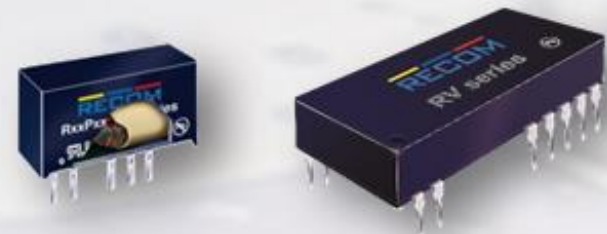**RH, RP, RGZ, RKZ, RV, RxxPxx, RxxP2xx**

- asymmetric dual output +15/-9V and +20/-5V and +15/-3V
- high isolation up to 6.4kVDC in SIP7, DIP14 & DIP24
- extremely low isolation capacitance
- efficiency up to 86%











# Selection Guide Overview



## DC/DC CONVERTERS

IGBT / SiC MOSFET

- Designed for IGBT/SiC driver circuits
- Up to 2 Watts
- Isolation voltages up to 6.4 kVDC
- Different pinout and package style
- Asymmetric output
- High efficiency
- High isolation
- Optional short circuit protection (P)
- RoHS compliant
- REACH compliant
- EN60950-1 certified
- 3 year warranty

Series	Power (W)	Vin (VDC)	Vout (VDC)	Isolation	Case / Dimensions	Certifications	Other features
 RH-xx1509D	1	5, 12, 24	+15/-9	3 or 4 kVDC/1 sec.	SIP7 19.6 x 10.2 x 7.05 mm (0.8" x 0.4" x 0.3")	EN60950-1	Asymmetrical outputs, designed for isolated IGBT drivers, operating temperature range: -40°C to +90°C, continuous short circuit protection (P)
 RP-xx1509D	1	5, 12, 24	+15/-9	5.2 kVDC / 1 sec.	SIP7 19.65 x 10.2 x 7.05 mm (0.8" x 0.4" x 0.3")	EN60950-1	Asymmetrical outputs, designed for isolated IGBT drivers, operating temperature range: -40°C to +85°C
 RxxP1509D	1	5, 12, 24	+15/-9	6.4 kVDC / 1 sec.	SIP7 19.5 x 12.5 x 9.8 mm (0.8" x 0.5" x 0.4")	EN60950-1	Asymmetrical outputs, designed for isolated IGBT drivers, operating temperature range: -40°C to +90°C, continuous short circuit protection (P)
 RGZ-xx1509D	2	5, 12, 24	+15/-9	3 or 4 kVDC/1 sec.	DIP14 19.9 x 10.0 x 7.1 mm (0.8" x 0.4" x 0.3")	EN60950-1	Asymmetrical outputs, designed for isolated IGBT drivers, operating temperature range: -40°C to +90°C, continuous short circuit protection (P)
 RKZ-xx1509D RKZ-xx2005D	2	5, 12, 24 5, 12, 15, 24	+15/-9 +20/-5	3 or 4 kVDC/1 sec.	SIP7 19.6 x 10.2 x 7.05 mm (0.8" x 0.4" x 0.3")	EN/IEC/UL60950-1 EN55022	Asymmetrical outputs, designed for isolated IGBT/SiC drivers, operating temperature range: -40°C to +100°C, continuous short circuit protection (P)
 R15P21503D	2	15	+15/-3	5.2 kVDC / 1 min.	SIP7 19.5 x 12.5 x 9.8 mm (0.8" x 0.5" x 0.4")	EN/IEC/UL60950-1 EN55022	Asymmetrical outputs, designed for isolated SiC drivers, operating temperature range: -40°C to +95°C
 RV-xx1509D	2	5, 12, 24	+15/-9	6 kVDC / 1 sec.	DIP24 32.4 x 14.7 x 11.1 mm (1.3" x 0.6" x 0.4")	EN60950-1	Asymmetrical outputs, designed for isolated IGBT drivers, operating temperature range: -40°C to +90°C
 RxxP22005D	2	5, 12, 24 5, 12, 15, 24	+15/-9 +20/-5	6.4 kVDC / 1 sec. 5.2 kVDC / 1 min.	SIP7 19.5 x 12.5 x 9.8 mm (0.8" x 0.5" x 0.4")	EN/IEC/UL60950-1 EN55022	Asymmetrical outputs, designed for isolated IGBT/SiC drivers, operating temperature range: -40°C to +95°C, continuous short circuit protection (P)

This Selection Guide only represents a variety of our most popular products. Please visit [www.recom-power.com](http://www.recom-power.com) or contact your local sales rep in case you do not find what you are looking for.

21

DC/DC CONVERTERS

## **SUMMARY:**

- **Different switching technologies demand different gate driver voltages.**
- **The easiest way to power the gate driver is via isolated DC/DC converters.**
- **There are asymmetric output DC/DC converters that are specifically designed to power gate drivers.**
- **The DC/DC supply is usually very low power, 2W or less, even if the application is switching many kW.**

# **RECOM**

## **We Power Your Products**

# Application Support & Tools

- EMC Lab for customer application measurements, EMC Seminars
- Application Notes and 7 white paper documents on the website  
3 special documents about IGBT, SiC and GaN Gate Driver Techn.
- New Product Selection Guide from April 2017
- New 3 rd. Edition of RECOM's DC/DC-Book of Knowledge  
(now new with chapter 10 about magnetics and transformers)
- Lots of different sample kits with datasheets directly available
- Use the support of our Top Distributor RUTRONIK from Breda

# Thanks a lot for your attention !!



- For any further information please contact the Rutronik Office as well, Takkebijsters 51, in 4817 BL Breda, Netherlands  
Mr. Fred Slebe: [Fred.Sleebe@rutronik.com](mailto:Fred.Sleebe@rutronik.com)
- Florian Boess, RECOM Electronic, [F.Boess@recom-power.com](mailto:F.Boess@recom-power.com)

20 juni 2017  
1931 Congrescentrum Den Bosch

**POWER**  
**ELECTRONICS**

2017