

Power Components
Testing & EMC
Power Applications
Power Research

POWER
ELECTRONICS 2017

20-06-17 - 1931 Congrescentrum Den Bosch

Vervorming in schakelende vermogensomzeters

dr.ir. B.J.D. Vermulst

20-06-2017

TU / **e** Technische Universiteit
Eindhoven
University of Technology

Where innovation starts



The issue with precision

What you expect the output is doing



What the output of the converter is actually doing


Accuracy, trueness and precision

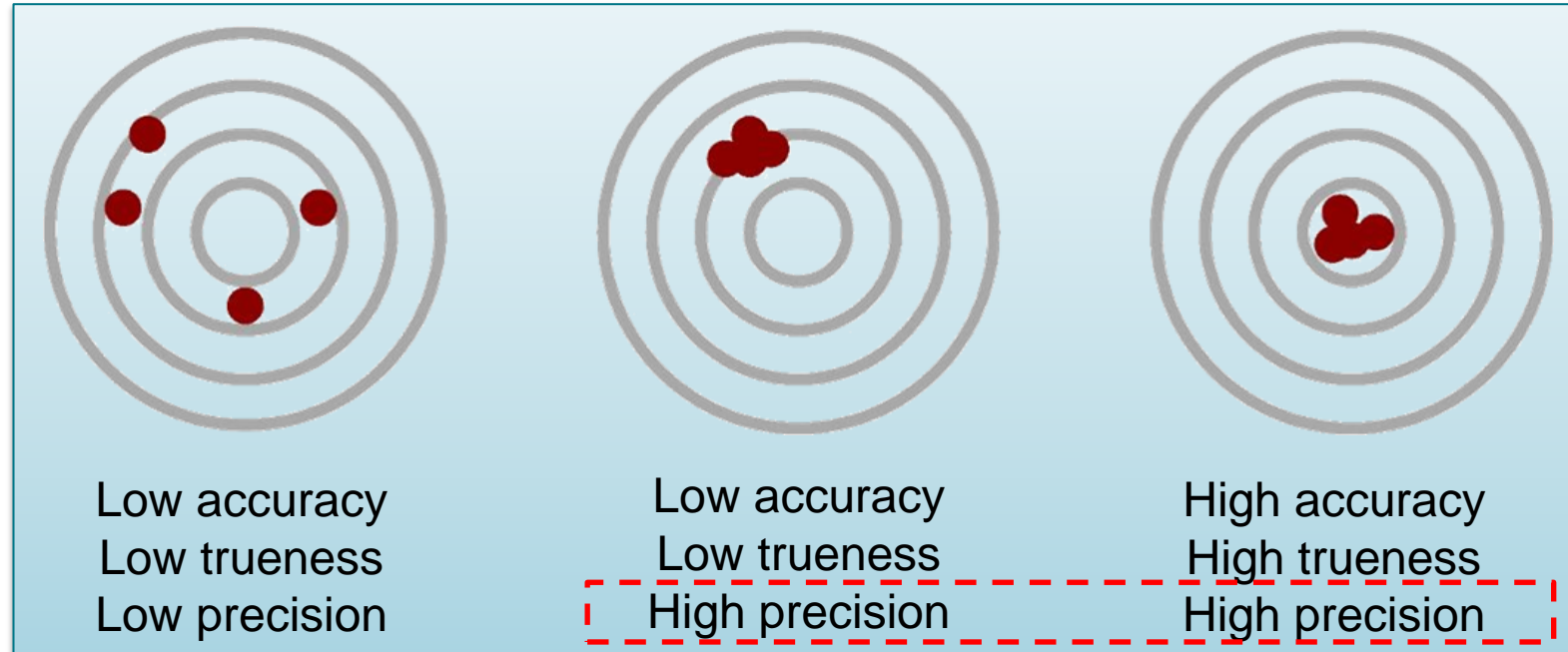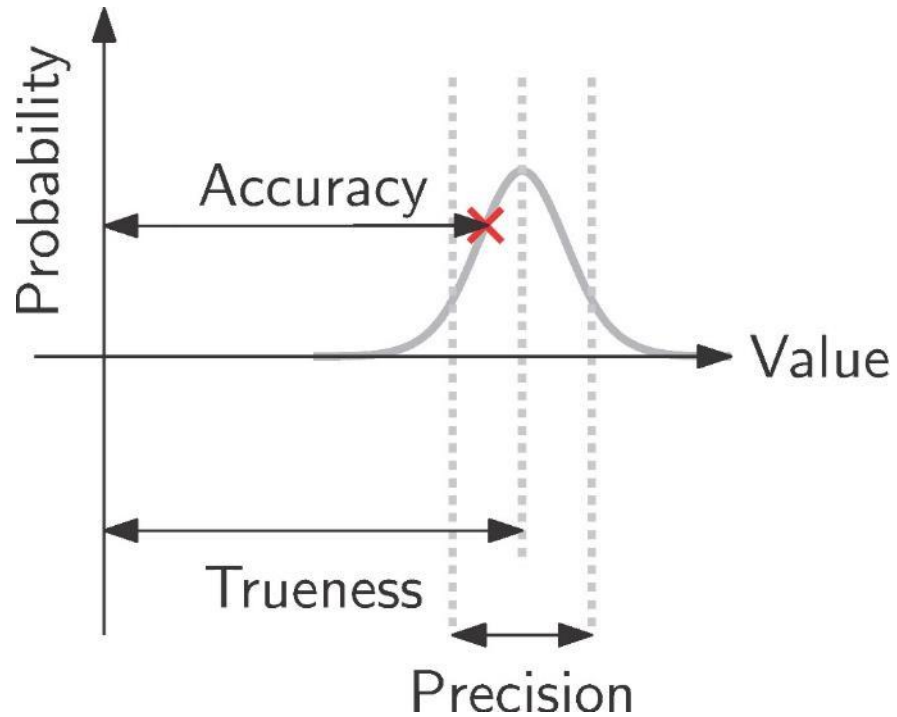

High precision is a necessary condition for high accuracy

High-precision power converter

- Generic block diagram:

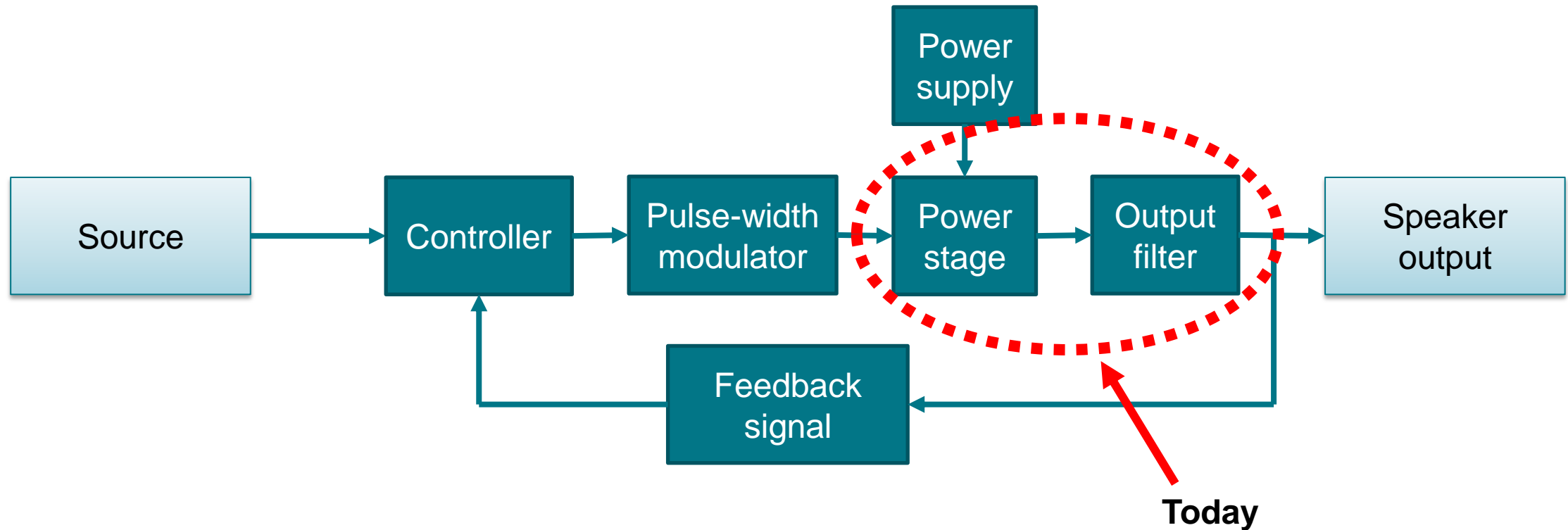

Distortion sources in power stage + filter

4

- Power stage
 - Dead-time
 - Non-linear on-state resistance & on-state resistance mismatch
 - Non-linear parasitic capacitances
 - Soft vs hard-switching
- Inductors
 - Saturation
 - Resistance variation
 - Hysteresis
- Capacitors
 - Voltage dependency
 - Relaxation

- Power stage
 - Dead-time
 - Non-linear on-state resistance
- Inductors
 - Saturation
 - Resistance variation



Today:


- Modeling techniques
- Results
- Conclusions

- Power stage
 - Dead-time
 - Non-linear on-state resistance


- Inductors
 - Saturation
 - Resistance variation

Dead-time distortion

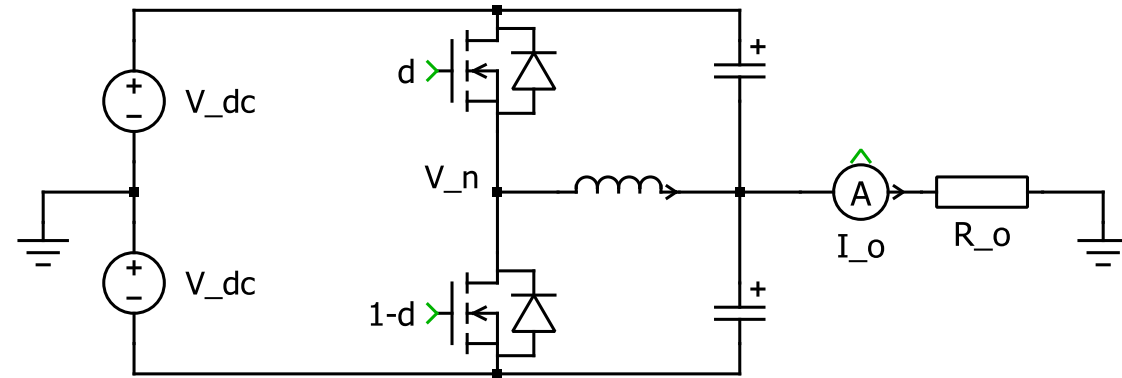- Dead-time: period of time where both transistors are off to prevent shoot-through
- When both transistors are off, the switched-node voltage is not forced to equal PWM output
 - *Voltage error occurs!*
- *Influence of dead-time on output THD?*



Average voltage error

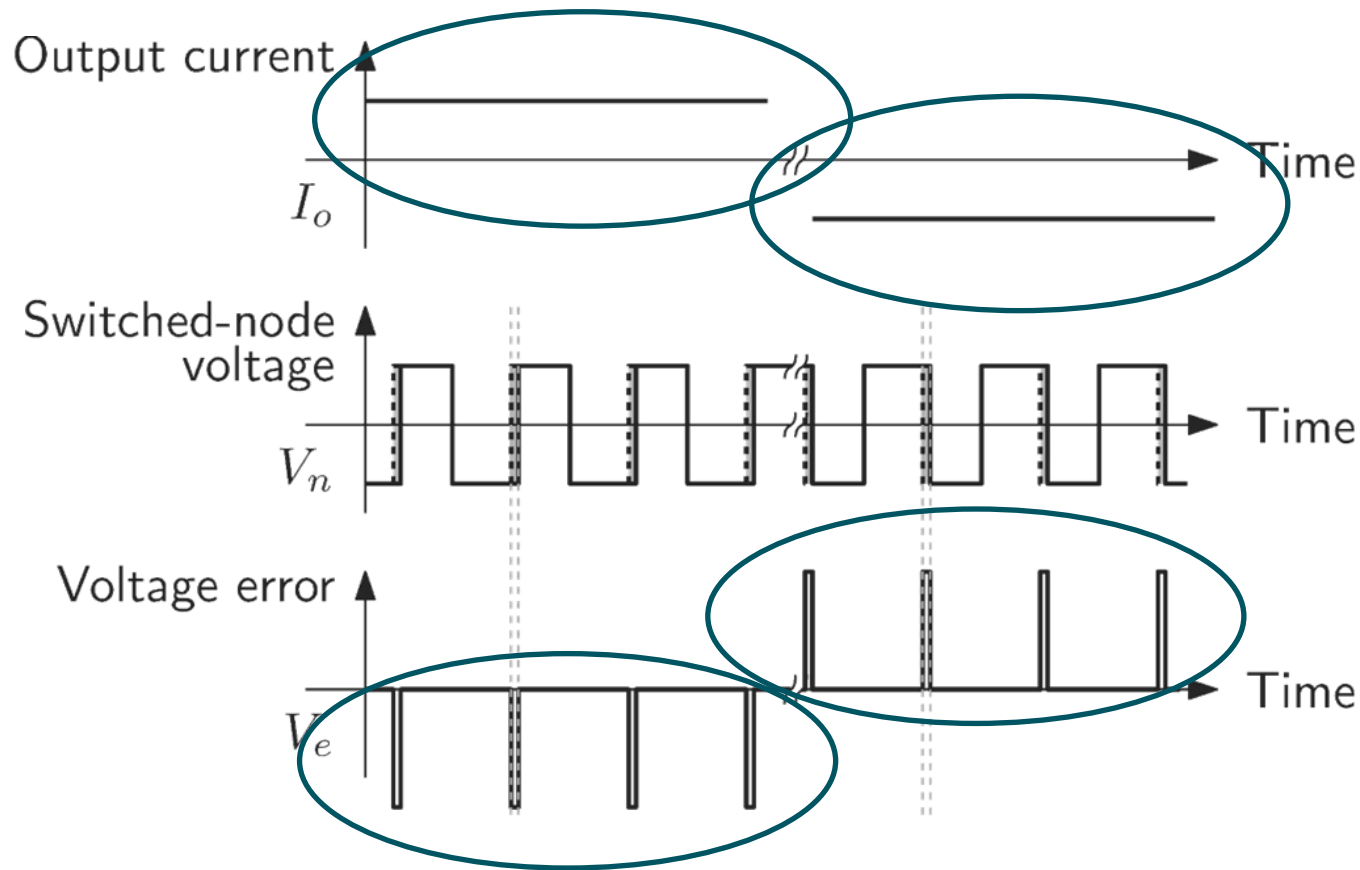

Average voltage error per switching cycle:


$$\langle V_e \rangle = -\frac{2t_{dt}V_{dc}}{t_p} \text{sign}(I_o)$$

with t_{dt} the dead-time, and t_p the period time.

Fourier-series of output voltage






Output voltage distortion

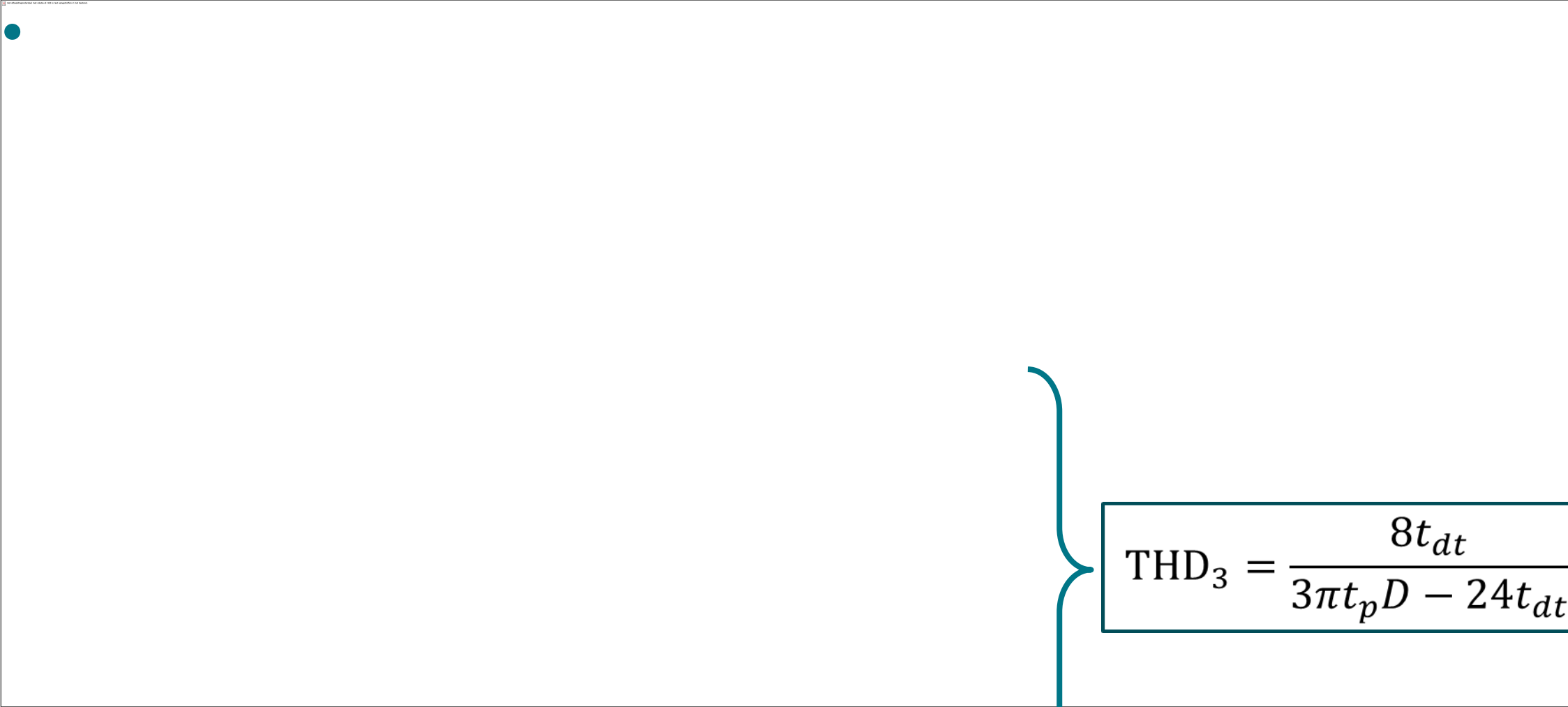
$$\text{THD}_3 = \frac{8t_{dt}}{3\pi t_p D - 24t_{dt}}$$

Calculation:


Simulation:

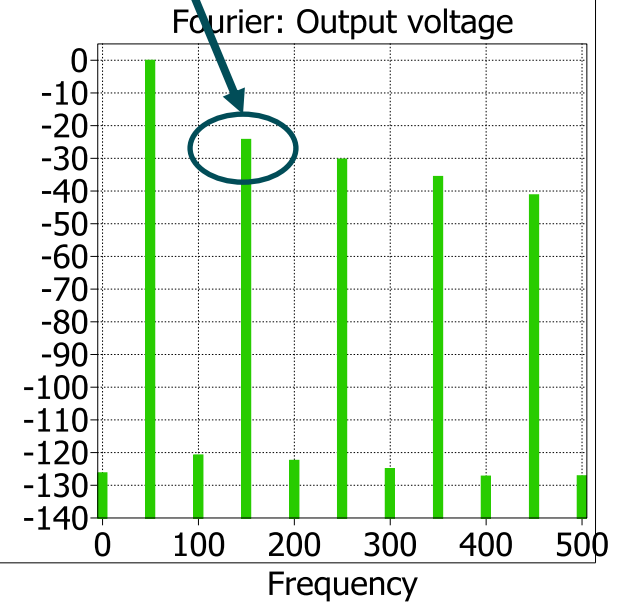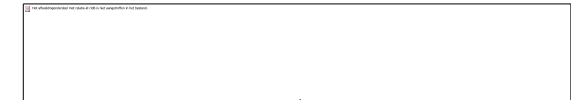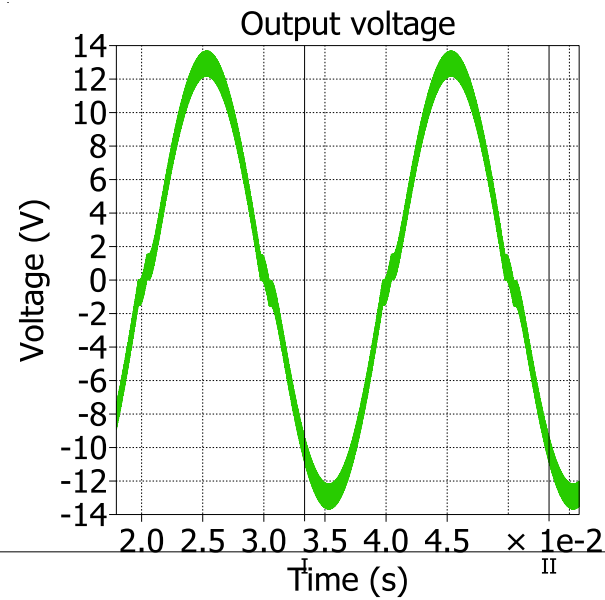

- Power stage
 - Dead-time
 - Non-linear on-state resistance

- Inductors
 - Saturation
 - Resistance variation

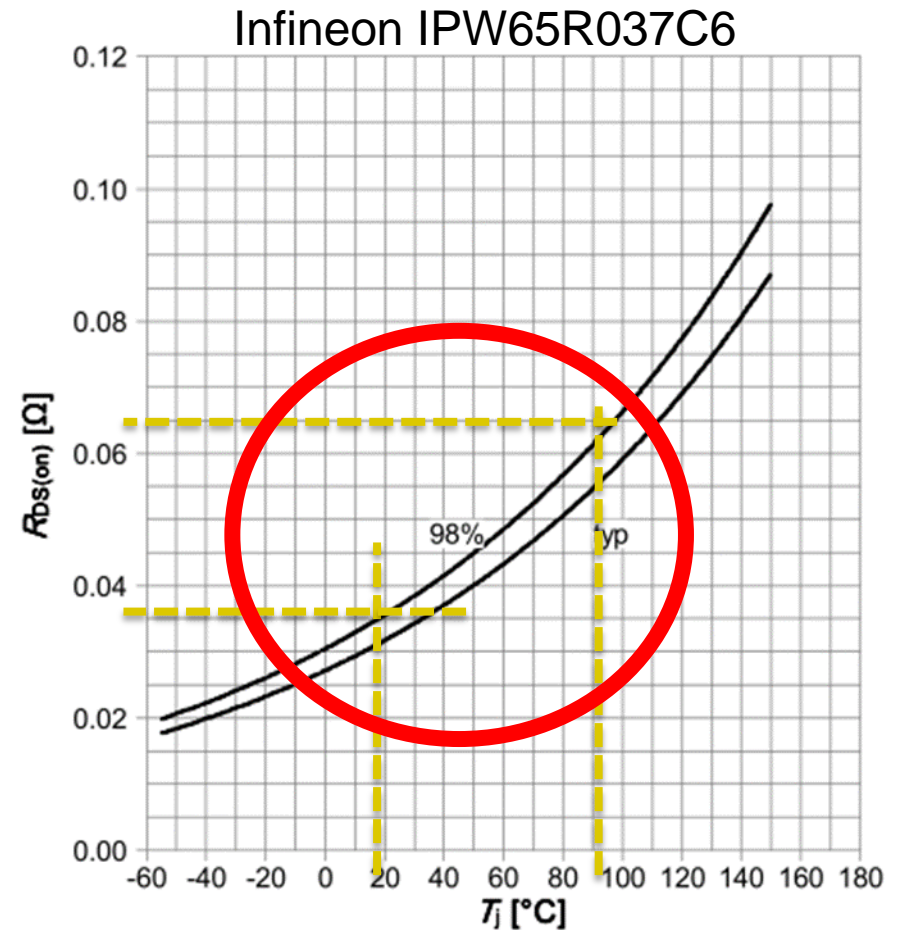- MOSFET on-state resistance varies with temperature
- *Influence of non-linear resistance on output THD?*



Dissipated power (1)


- Determine first-order Taylor-approximation:

- $R_{ds,fit}(T) = R_{ds}(T_{heatsink}) + \frac{dR_{ds}}{dT_j}(T - T_{heatsink})$

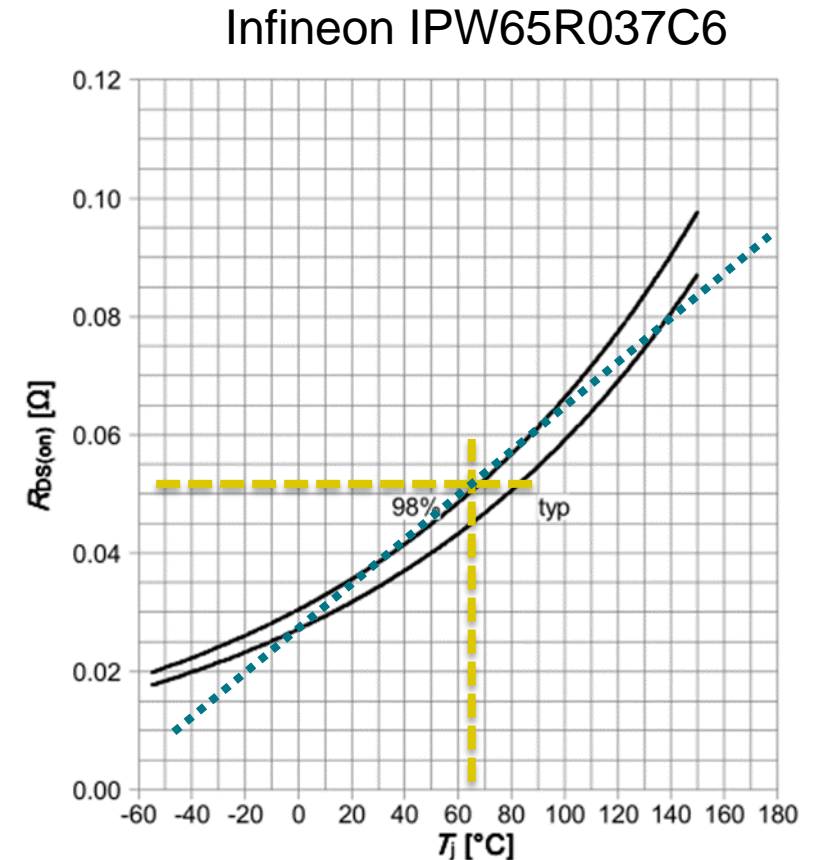- Example:

$T_{heatsink} = 60^\circ\text{C}$ for Infineon IPW65R037C6 MOSFET, then:

- $R_{ds}(T_{heatsink}) \approx 0.048 \Omega$
- $\frac{dR_{ds}}{dT_j} \approx 350 \cdot 10^{-6} \Omega/\text{K}$




Dissipated power (2)

- The top MOSFET junction dissipated power equals

$$P_{top,sw}(t) = I_{top,sw}^2(t) R_{ds} = \frac{D^2 V_{dc}^2 R_{ds}}{2(R_o + R_{ds})^2} \cos^2(\omega_0 t) (1 + D \cos(\omega_0 t))$$

- The **second harmonic ($2\omega_0$)** is dominant for small D , and equals
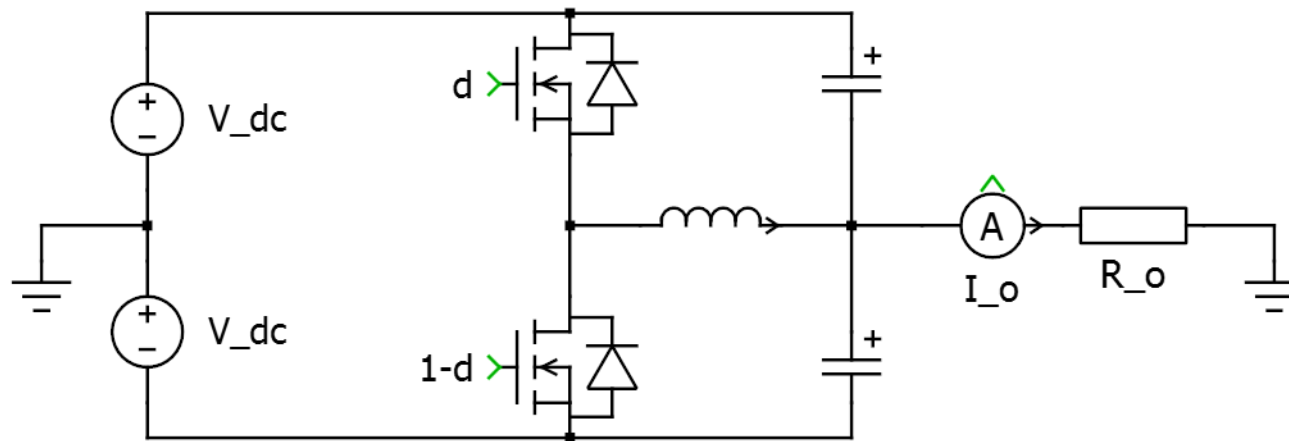
$$P_{top,sw,f2}(t) = \frac{D^2 V_{dc}^2 R_{ds}}{4(R_o + R_{ds})^2} \cos(2\omega_0 t)$$




Half-bridge topology with output filter


Transistor thermal model

- Thermal model

Infineon IPW65R037C6

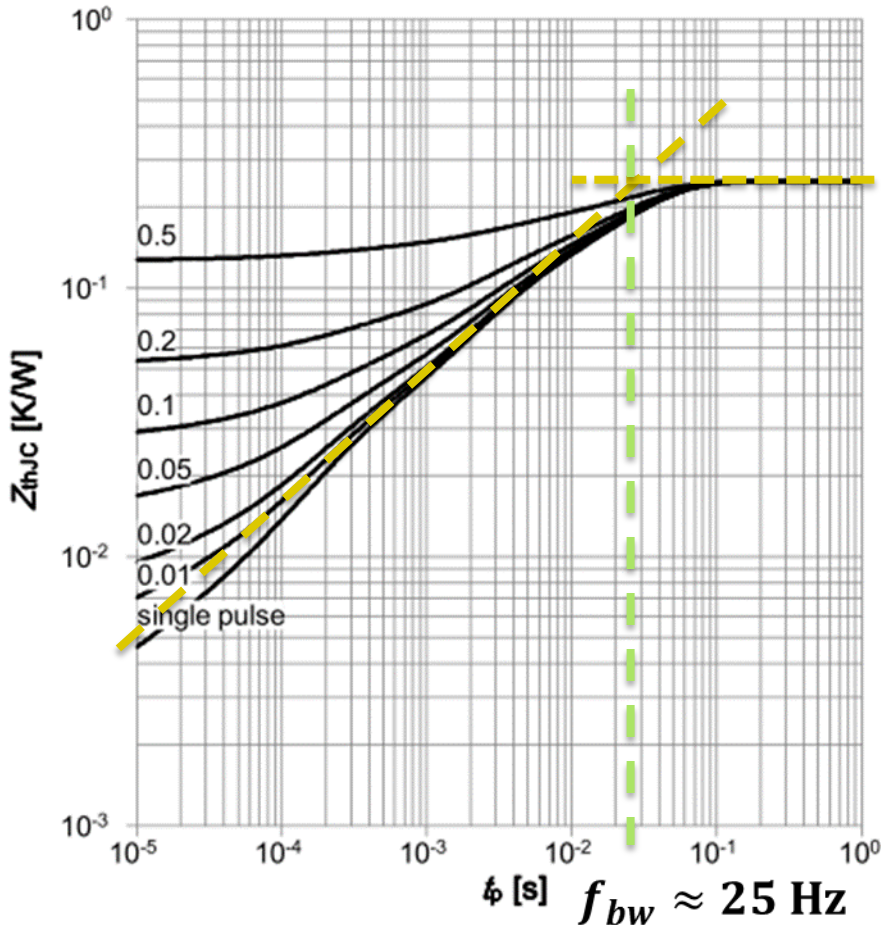

$R_{JC} \approx 0.25 \text{ K/W}$

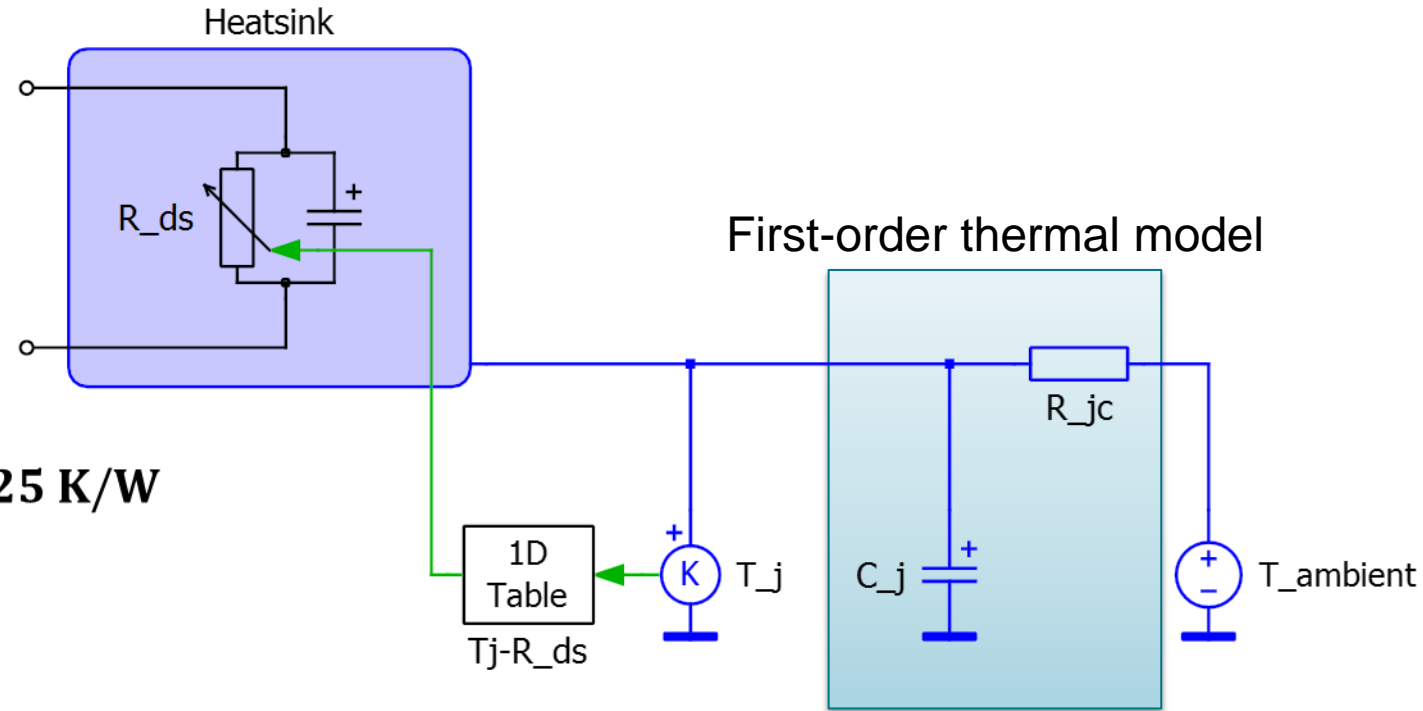


$$2\pi f_{bw} R_{JC} C_J = 1$$

Therefore it holds that

$$C_J = \frac{1}{2\pi f_{bw} R_{JC}}$$

Output voltage distortion

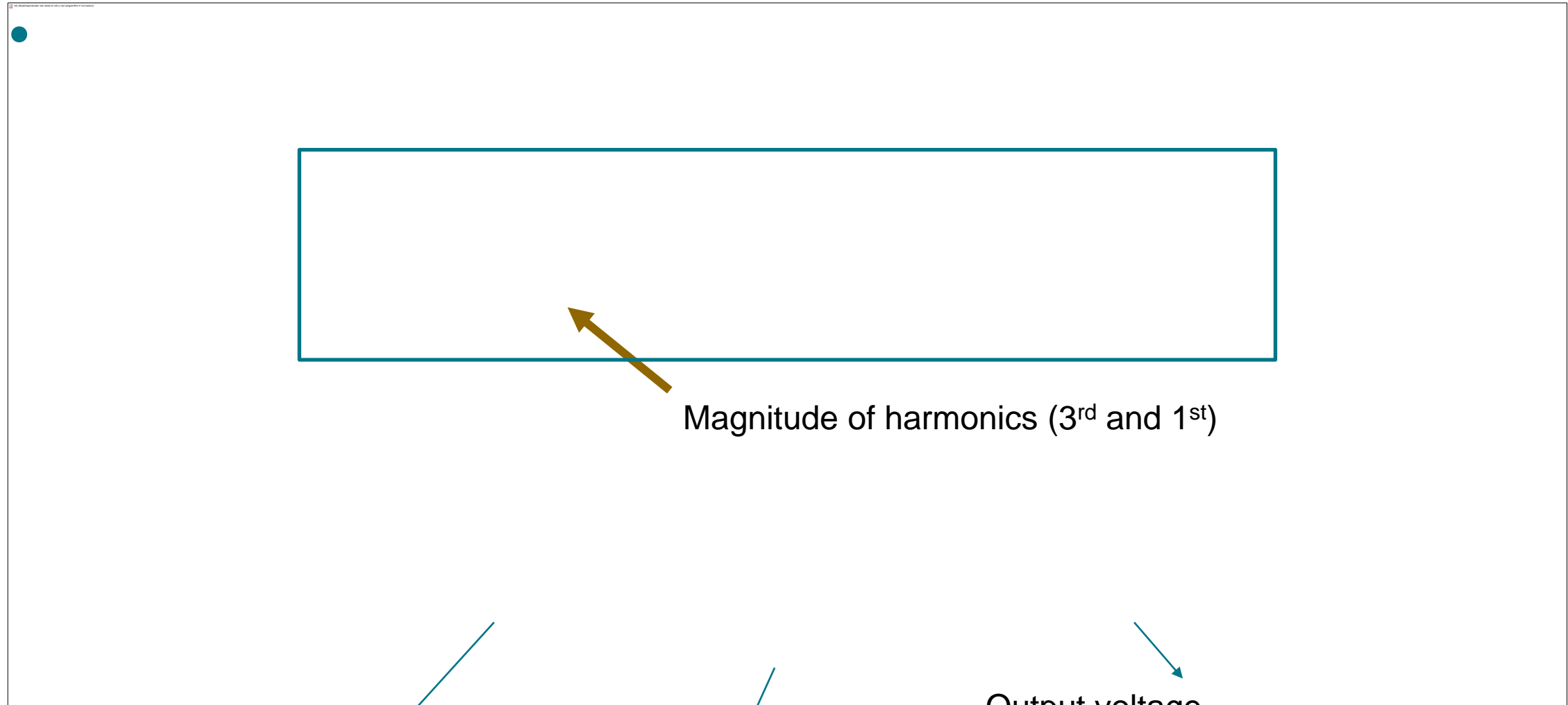

Magnitude of harmonics (3rd and 1st)

From datasheet


From thermal model

Output voltage
(linearized resistor divider)

5 Hz excitation in 1 Ohm load

Calculation:




Simulation:

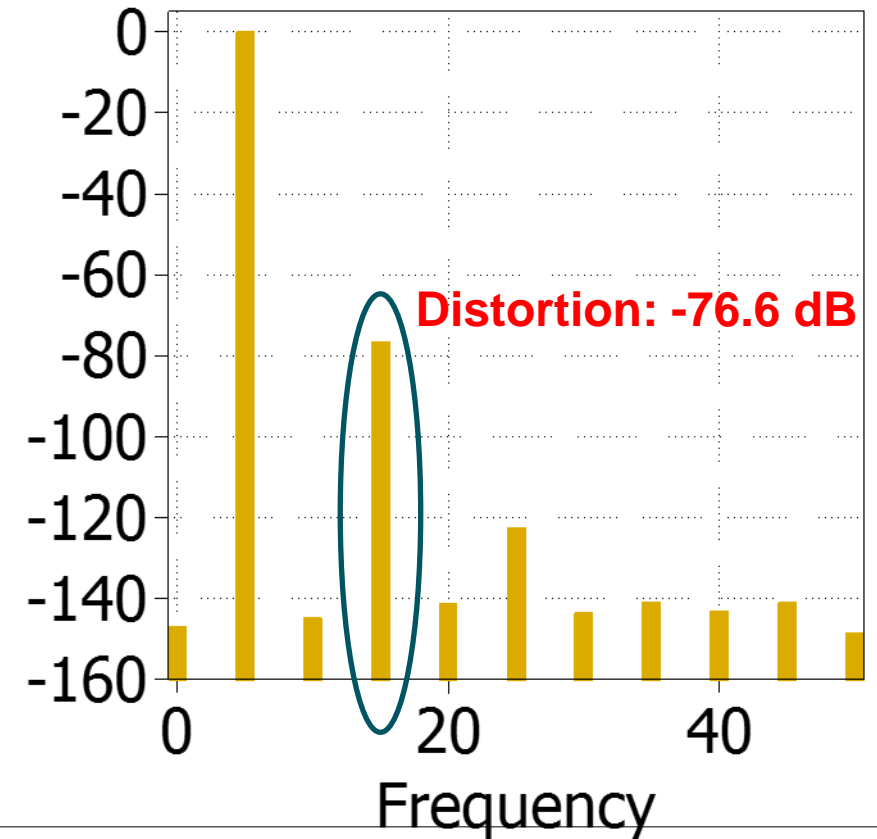

Note: fifth harmonic (-122 dB) can be found by using a second-order Taylor approximation at slide 16.

- Power stage
 - Dead-time
 - Non-linear on-state resistance
- Inductors
 - Saturation
 - Resistance variation

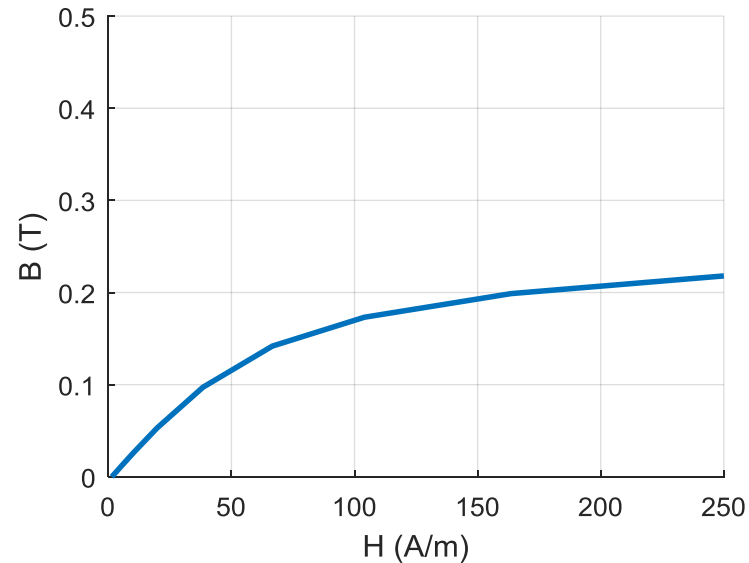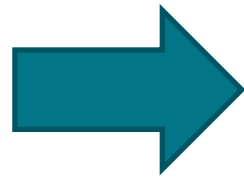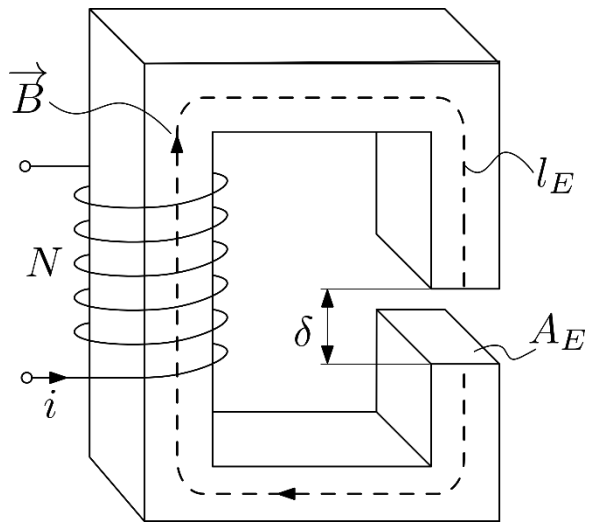- Core material is non-linear → distortion!



Procedure steps:

1. Determine swing of inductance
2. Find resulting voltage error
3. Calculate third harmonic magnitude

Determining inductance swing (1)

- Sinusoidal excitation: determine inductance at $H = 0$ and $H = H_E$

1. Determine inductance with load line technique

$$\mathcal{F} = Ni = H_E l_E + H_\delta \delta$$

$$B_\delta = B_E$$

therefore

$$H_\delta = \frac{B}{\mu_0}$$



$$H_E = -\frac{\delta}{\mu_0 l_E} B + \frac{Ni}{l_E}$$

N=number of turns
i=current

Core

Air gap

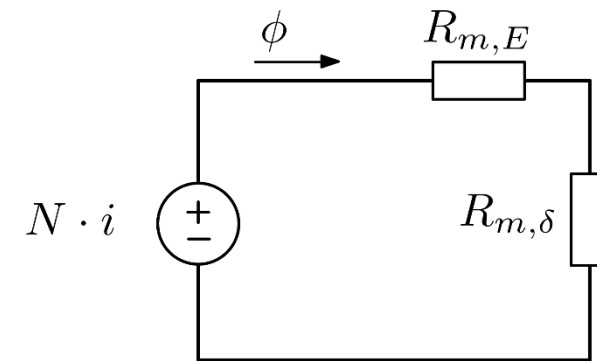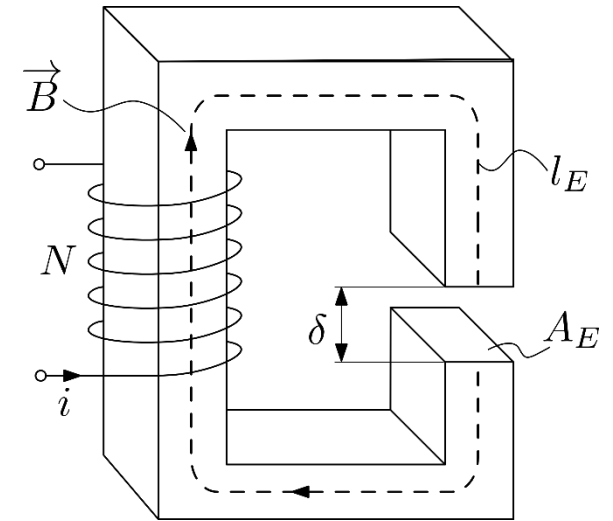Load line equation: all possible solutions for H as function of B with given geometry and operating current.




Determining inductance swing (2)

2. Determine BH-curve of material using


$$\int dB = \int \mu dH \rightarrow B = \int \mu_0 \mu_r dH$$

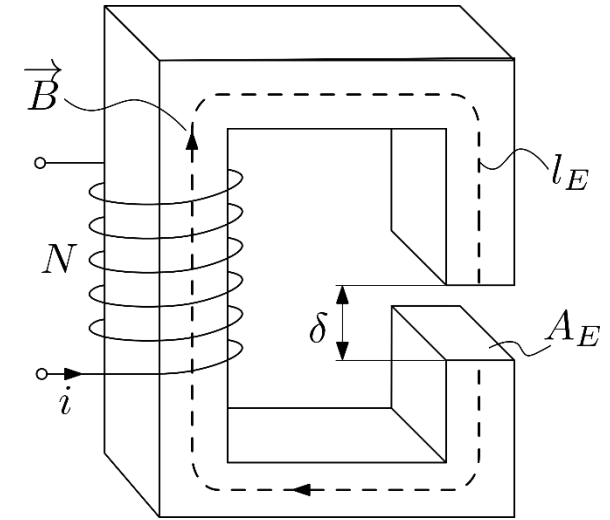3. Find intersection of load line with BH-curve


$$H_E = -\frac{\delta}{\mu_0 l_E} B + \frac{Ni}{l_E}$$



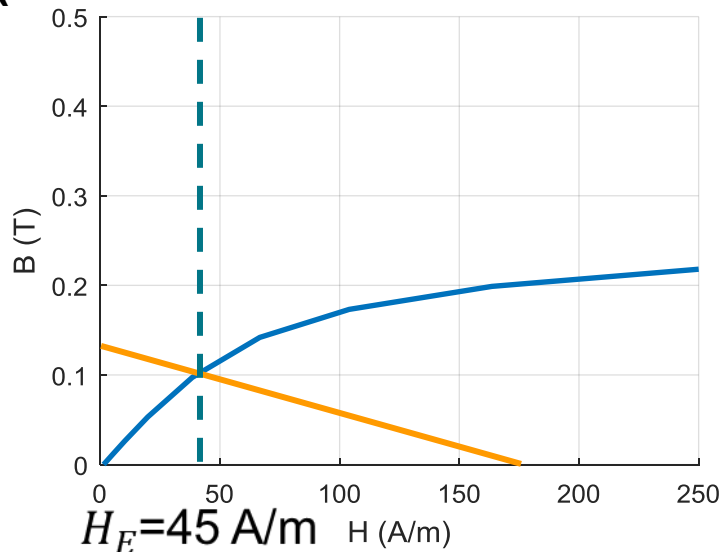3C90 BH-curve
(calculated from saturation curve)



3C90 saturation curve
(from datasheet)

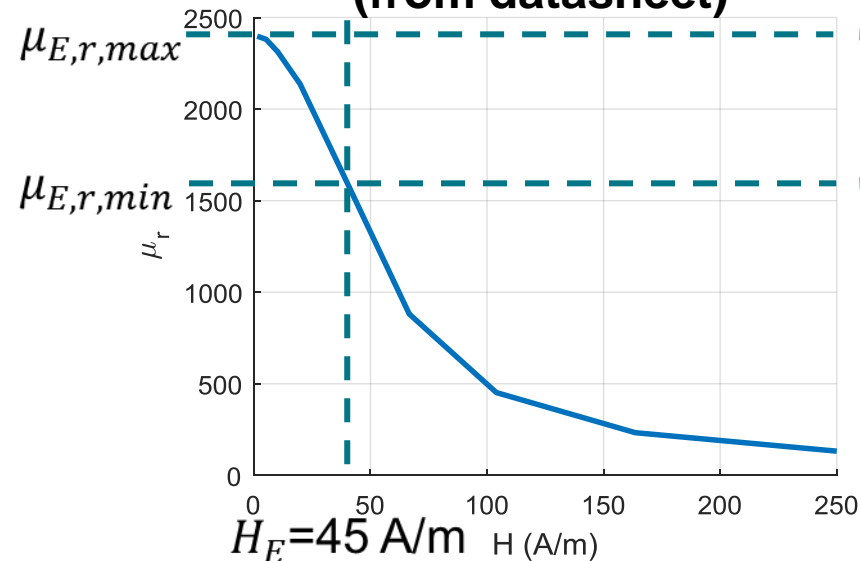

mu_r swing -> inductance swing

Voltage error

- Finding inductor harmonic distortion:

- Output current:

$$i_o = I_o \sin(\omega_o t)$$

- Voltage over inductor:



$$V_L = L \frac{di_o}{dt}$$

- Distortion = difference from ideal inductor:

$$V_{\text{error}} = \Delta L \frac{di_o}{dt}$$

maximum at maximum current maximum at zero current

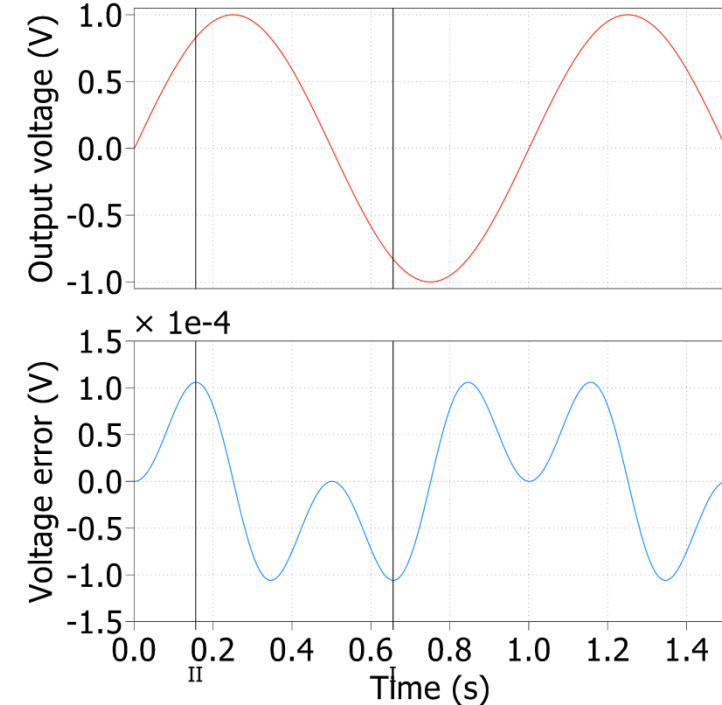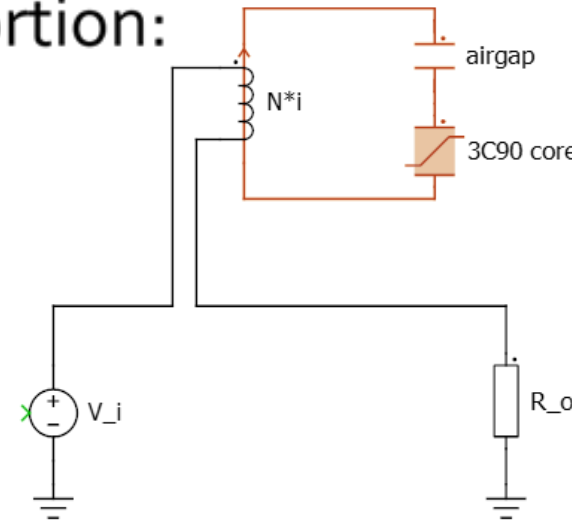- Maximum of V_{error} occurs at $i_o \approx 0.8I_o$ (see graph)



Harmonic distortion

Note we assume resistive behavior here!

- Distortion equal to

$$V_{\text{error}} = \Delta L \frac{di_o}{dt} \quad \frac{di_o}{dt} = I_o \omega_o \cos(\omega_o t) \approx \frac{\omega_o V_i \cos(\omega_o t)}{R_o}$$

- At $i_o = 0.8I_o$:

$$\frac{di_o}{dt} = \frac{\omega_o V_i \cos(\arcsin(0.8))}{R_o} = \frac{0.6\omega_o V_i}{R_o}$$



- Maximum error therefore:

$$V_{\text{error}} = (L_{\text{max}} - L_{\text{min}}) \frac{0.6\omega_o V_i}{R_o}$$

- Harmonic distortion using third harmonic magnitude:

$$\text{THD}_3 = \frac{3\sqrt{3}V_{\text{error}}}{8V_i}$$

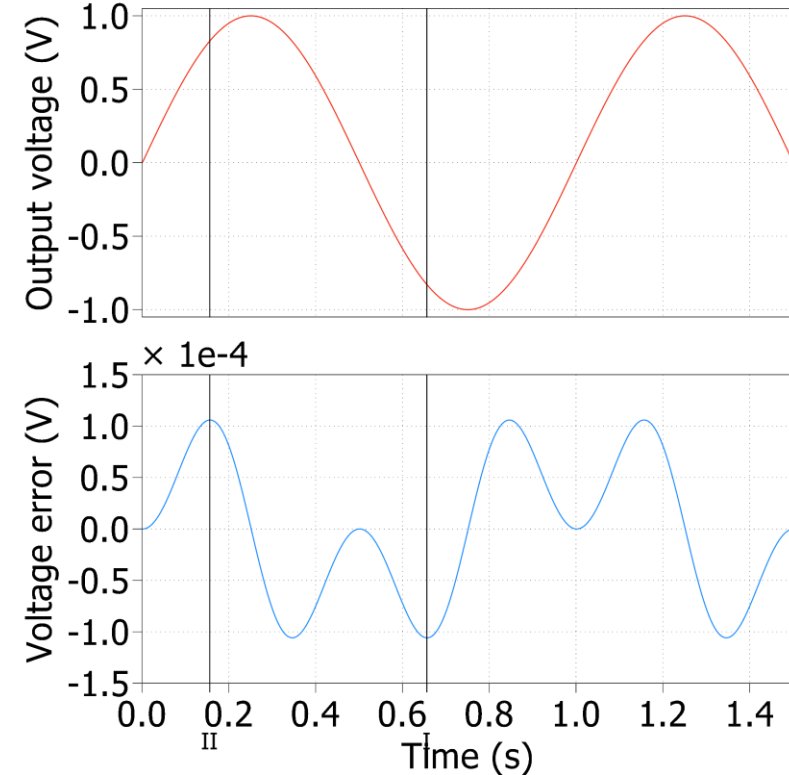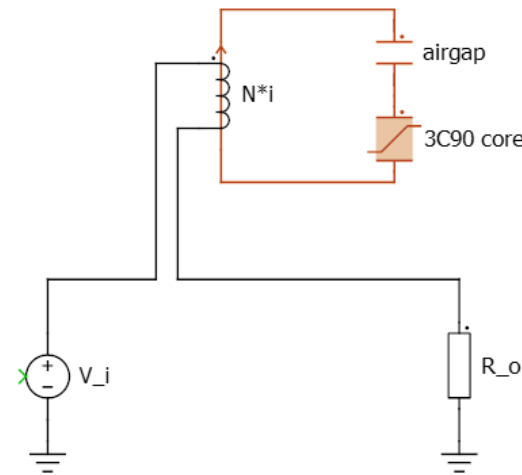First harmonic and third harmonic have equal magnitude.
 Ratio peak error and harmonic magnitude $\frac{8}{3\sqrt{3}}$.




Calculation result:

Result from calculations in previous slides:




Accurate!

Simulation diagram:

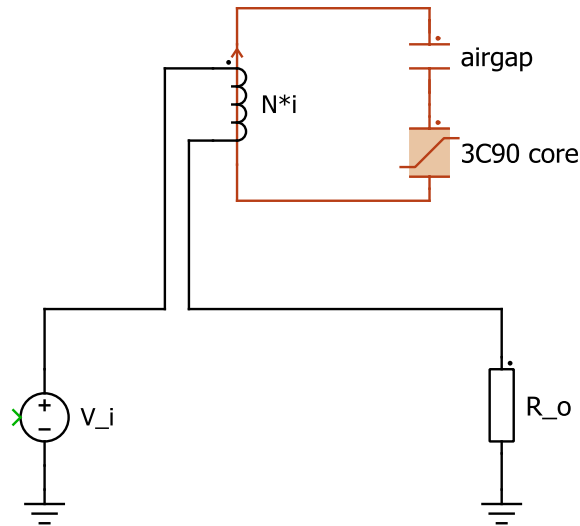

Simulation result:


MATLAB Simulink + PLECS simulation

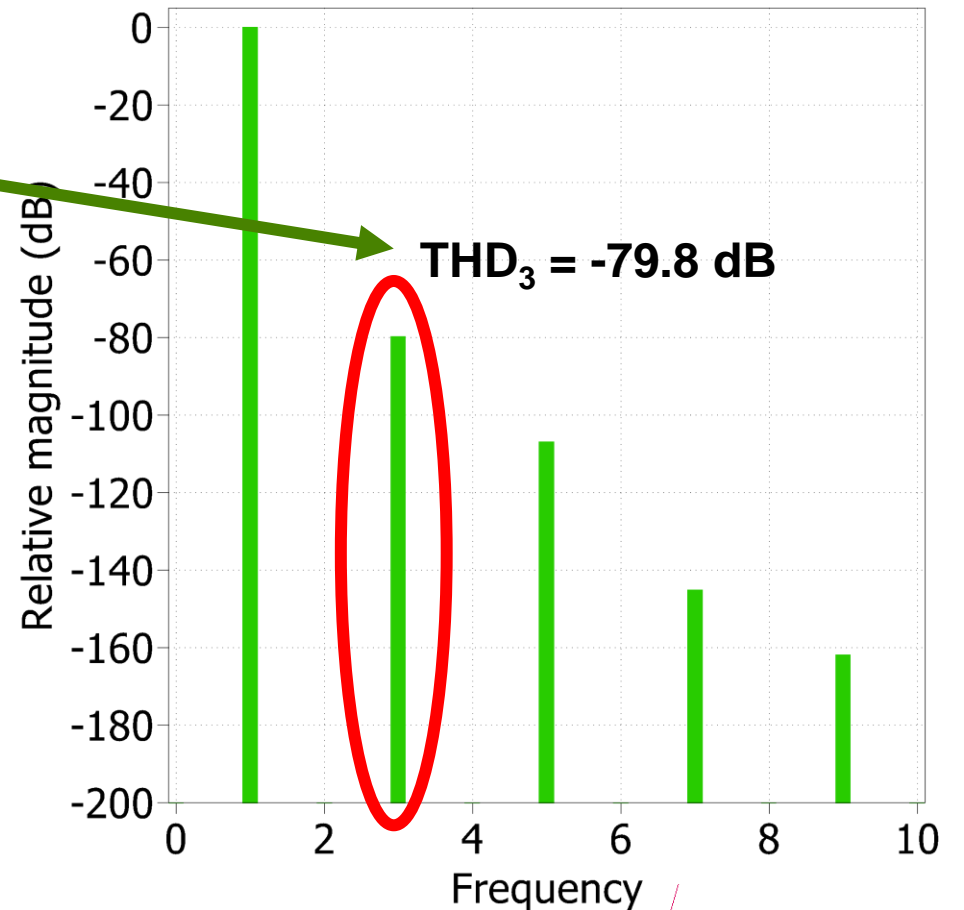

- Power stage
 - Dead-time
 - Non-linear on-state resistance
- Inductors
 - Saturation
 - Resistance variation

Winding thermal model


- Assume first-order thermal model

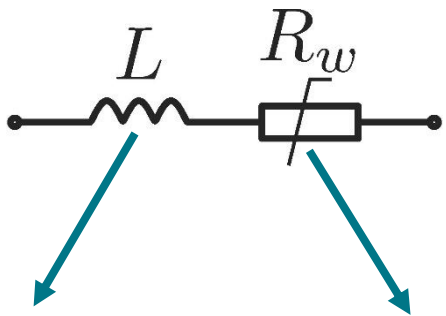

“Ideal” inductor

Parasitic electric resistance

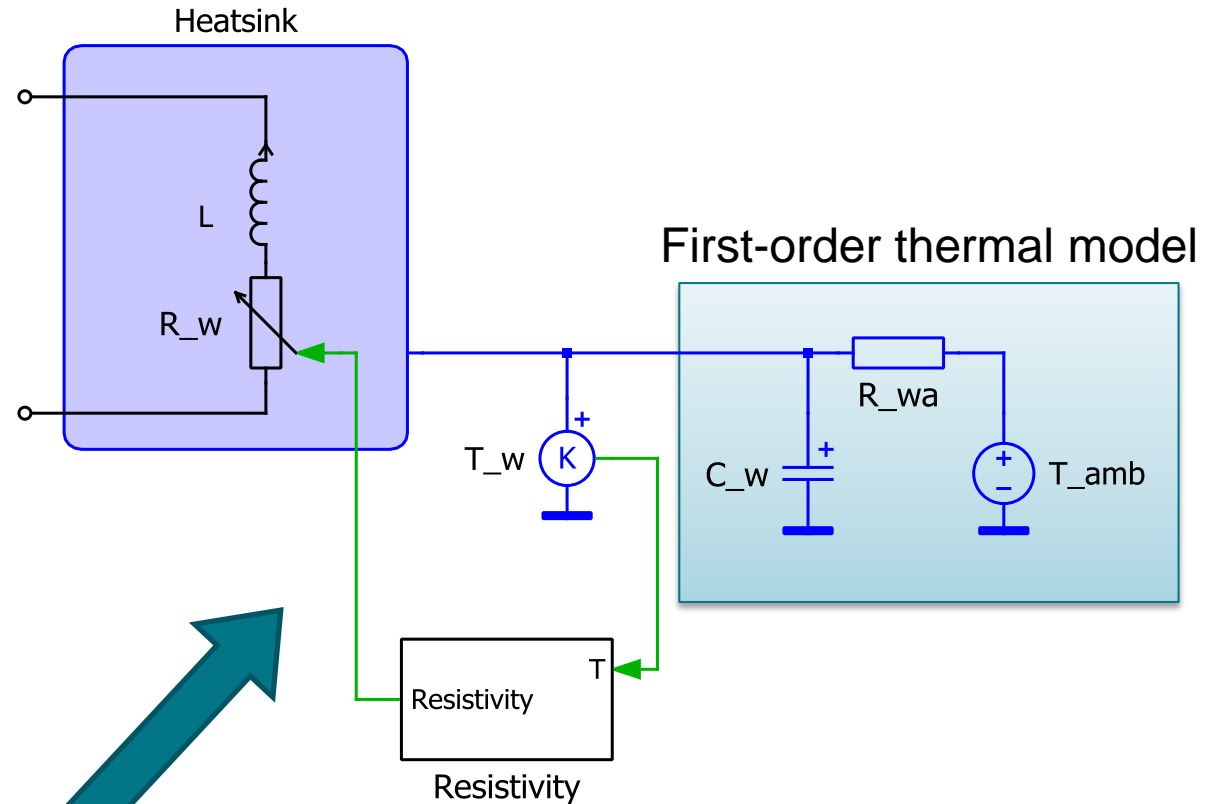Copper mass → thermal capacity
Winding surface area → thermal resistance
Electrical resistance is temperature dependent!



Output voltage distortion

- The THD caused by non-linear resistance of winding equals

$$\text{THD}_3(t) = \frac{V_{o,f3}}{V_{o,f1}} = \frac{R_{w,swing}}{2(R_o + R_{w0}) - R_{w,swing}}$$

Magnitude of harmonics (3rd and 1st)

with


$$R_{w,swing} = \alpha R_{w0} \left(\frac{R_{wa}}{\sqrt{4\omega_o^2 C_w^2 R_w^2 + 1}} \right) \left(\frac{\hat{I}^2 R_{w0}}{2} \right)$$


Calculation results:



Simulation results:

Output voltage spectrum

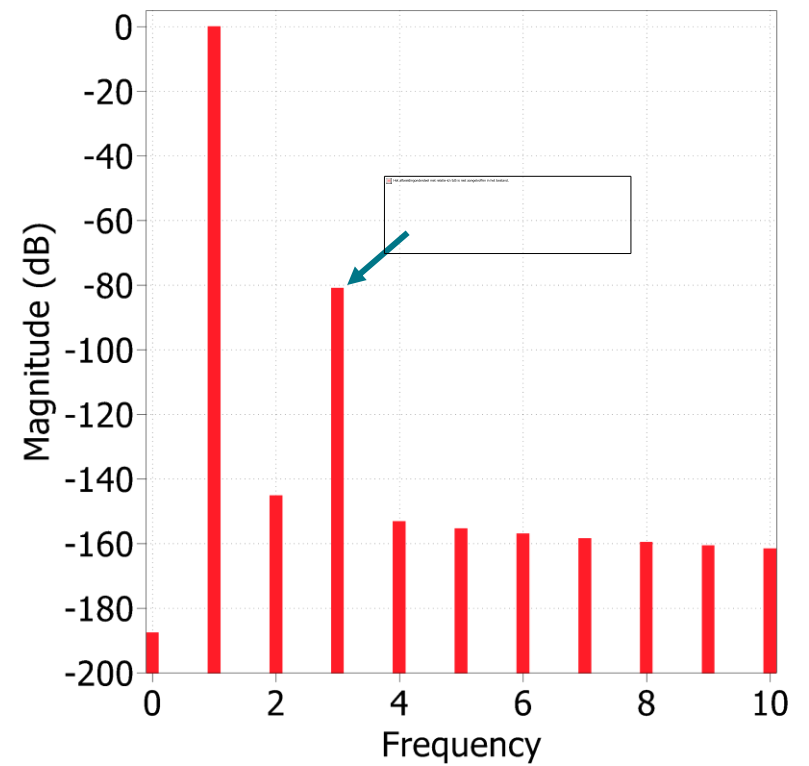


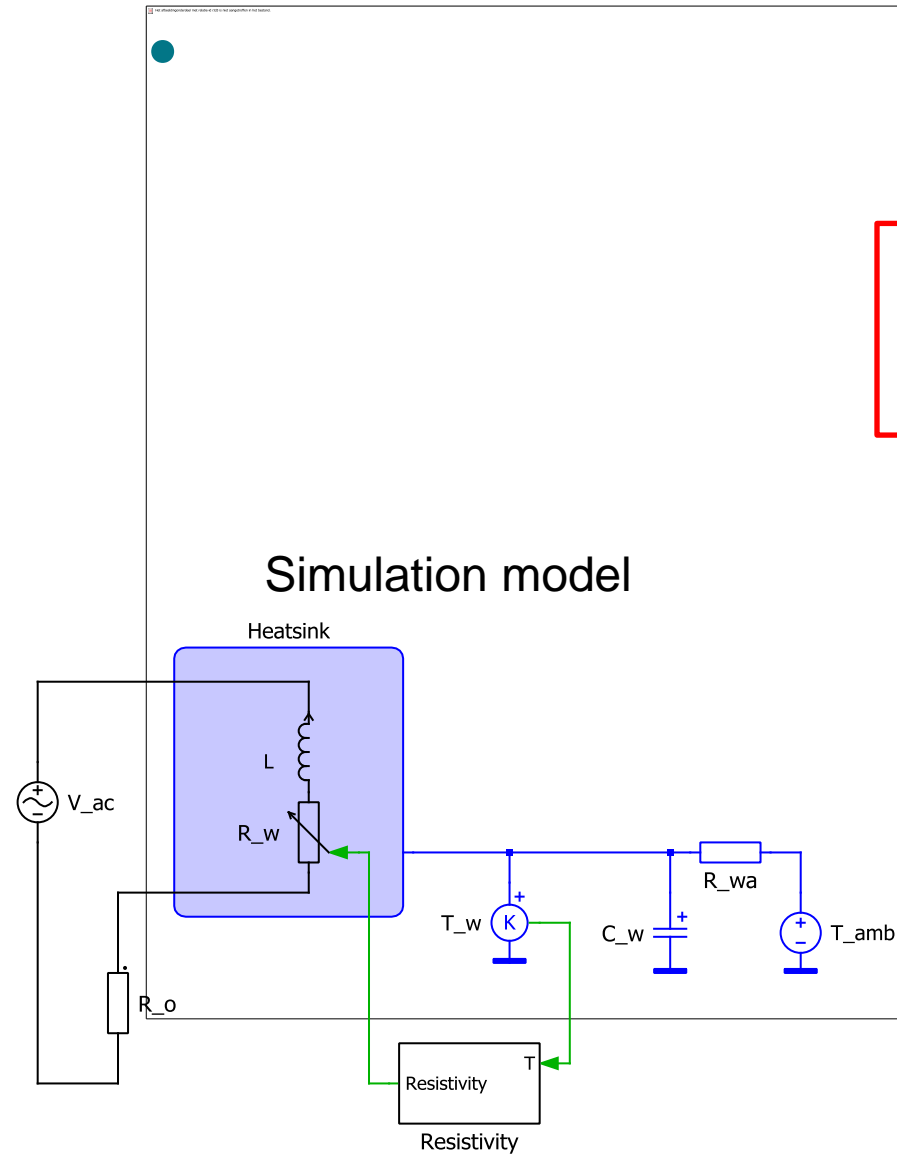


High dissipation in inductor is required to reach significant distortion



Results

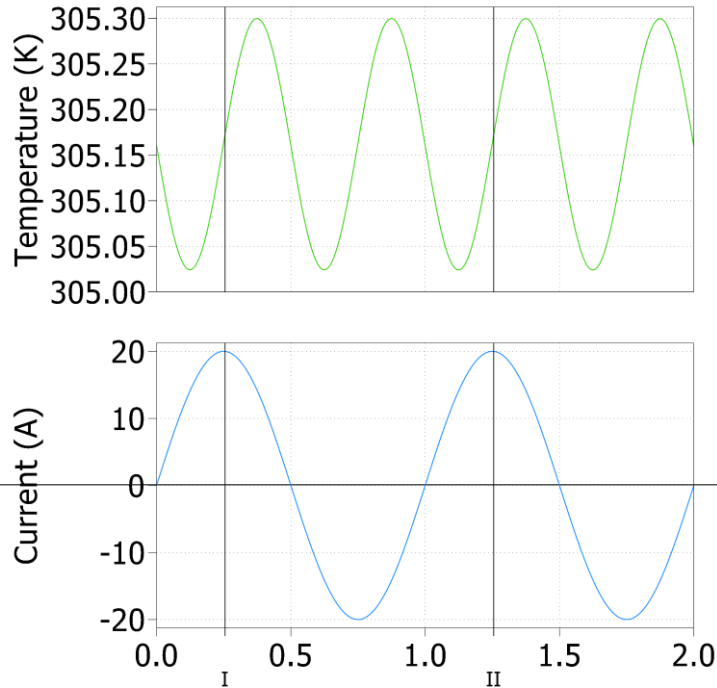

Output voltage spectrum

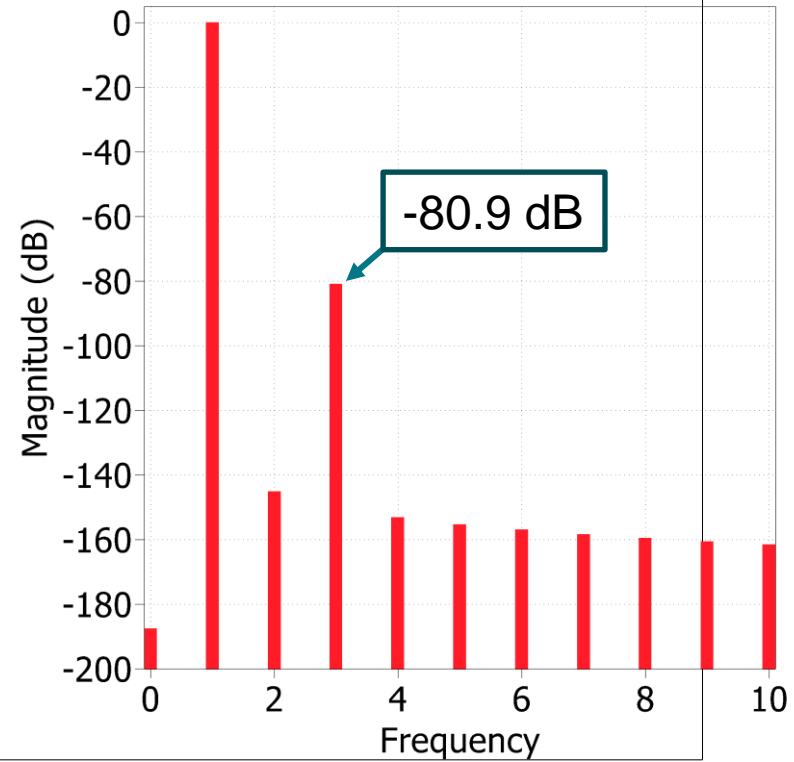

- High-precision requires accurate models of all converter components
- Various non-linear effects modeled and validated with good results
- Most significant effect in most scenarios is dead-time
- Inductor core hysteresis is not covered



“That’s all Folks!”

Any questions?