

Acradac

EMC Training and Consultancy

www.acradac.com
emc@acradac.com

EMC: Common mode stromen veroorzaakt door Power Devices,
weet jij waar ze lopen?

Lex de Rijck

20 juni 2017
1931 Congrescentrum Den Bosch

POWER
ELECTRONICS


2017

Common mode currents

- **Cause EMI emissions (both conducted and radiated)**
- **Cause self-contamination, which can lead to malfunctions**

Basic EMI principle


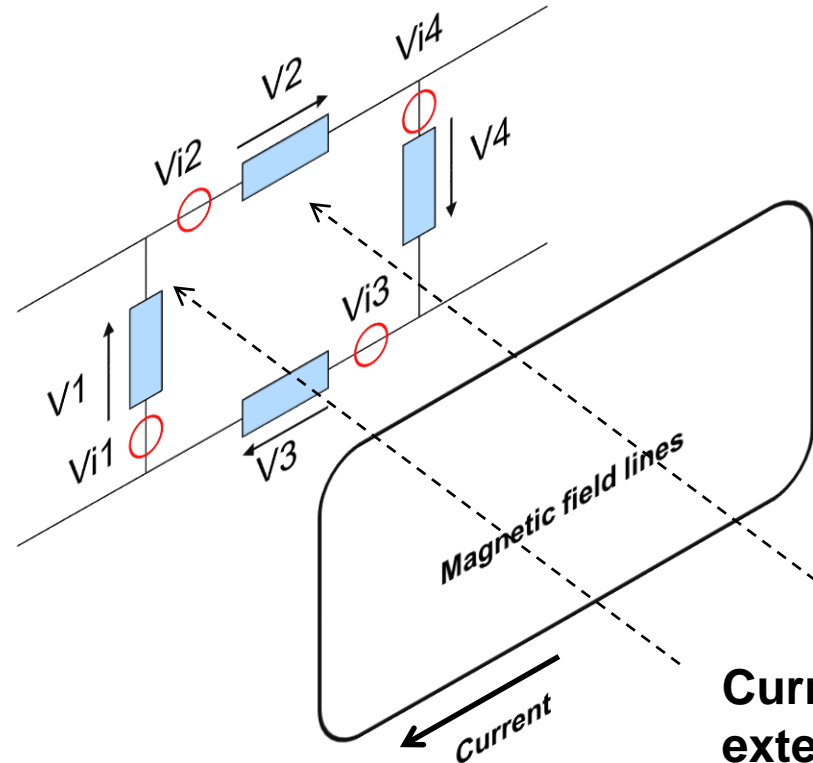
Big loops are bad for EMC and should be as small as possible (for both emission and immunity)



$$\oint E \cdot dl = - \frac{d\Phi}{dt}$$

Current loop in vicinity or an external field (Wifi, GSM, GPS, Bluetooth, RF-ID, Radio 3, home automation, radio-amateurs, CB, etc...)

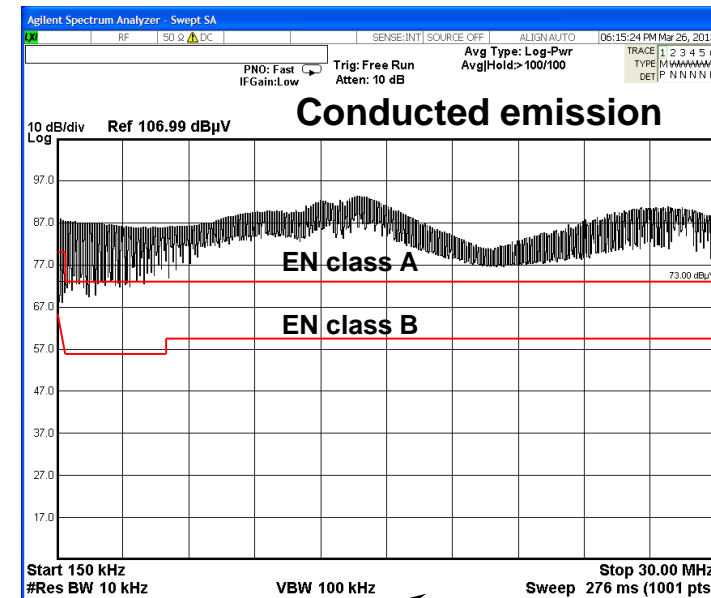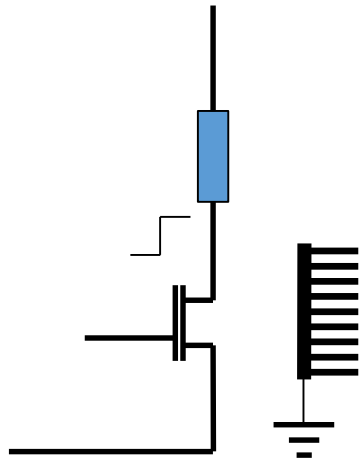Standard issue: capacitive coupling between switching device and heat sink





- Filters
- Ferrite beads
- Gaskets
- Shielding


Are they necessary?

- 
- Filters
 - Ferrite beads
 - Gaskets
 - Shielding


Example 1: power factor corrector

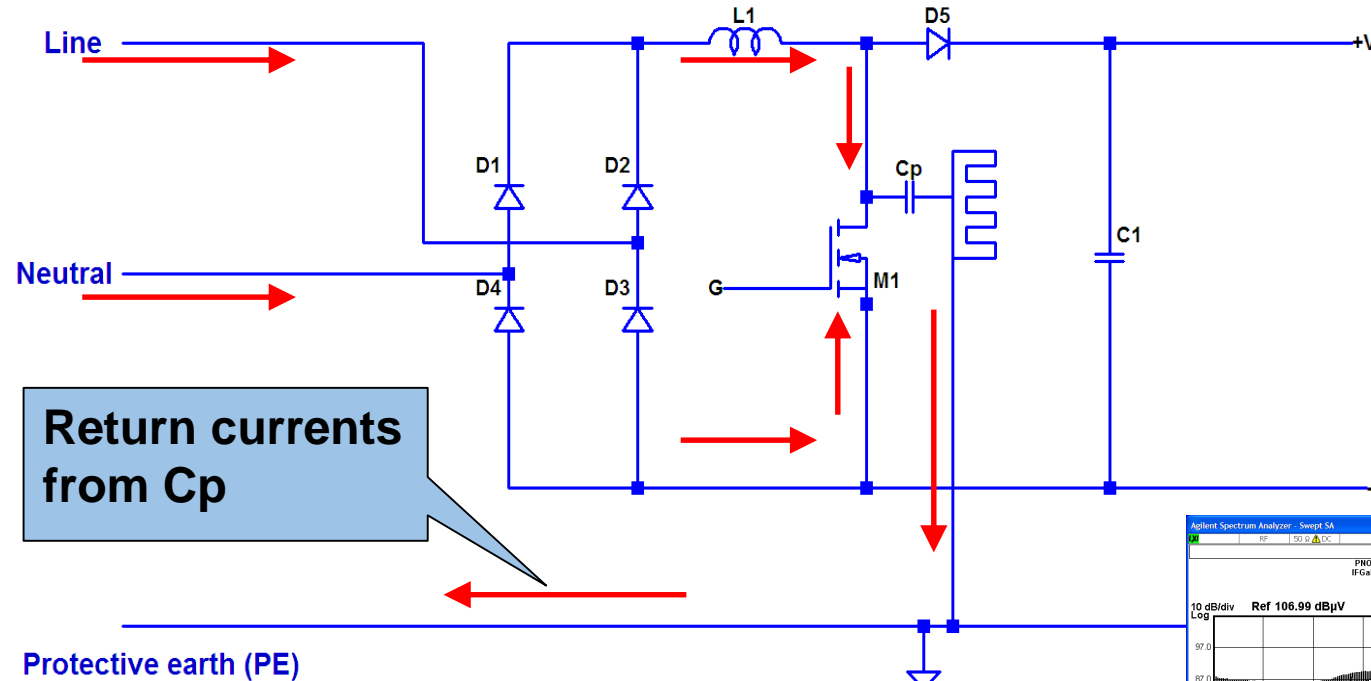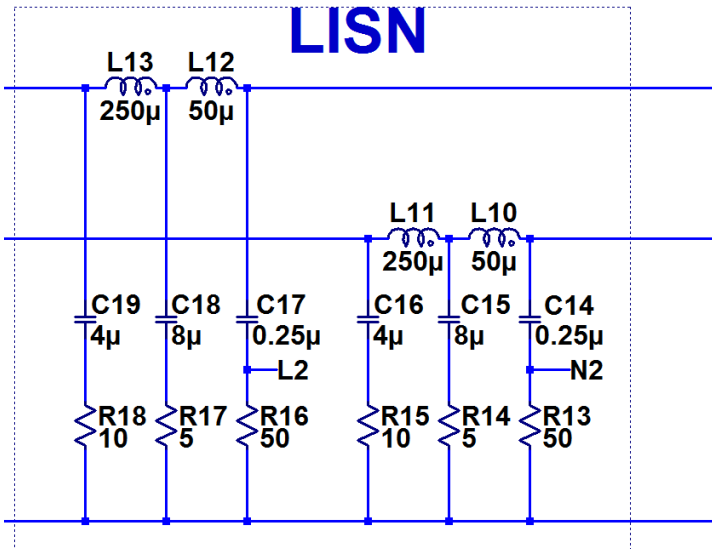

Generally, the heat sink is connected to the ground.
This is the worst possible scenario

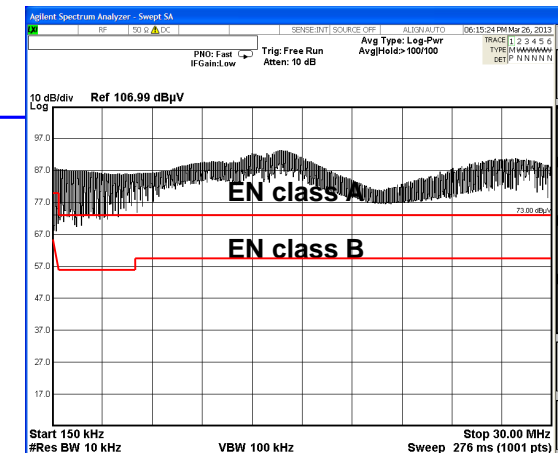

Example 1: power factor corrector

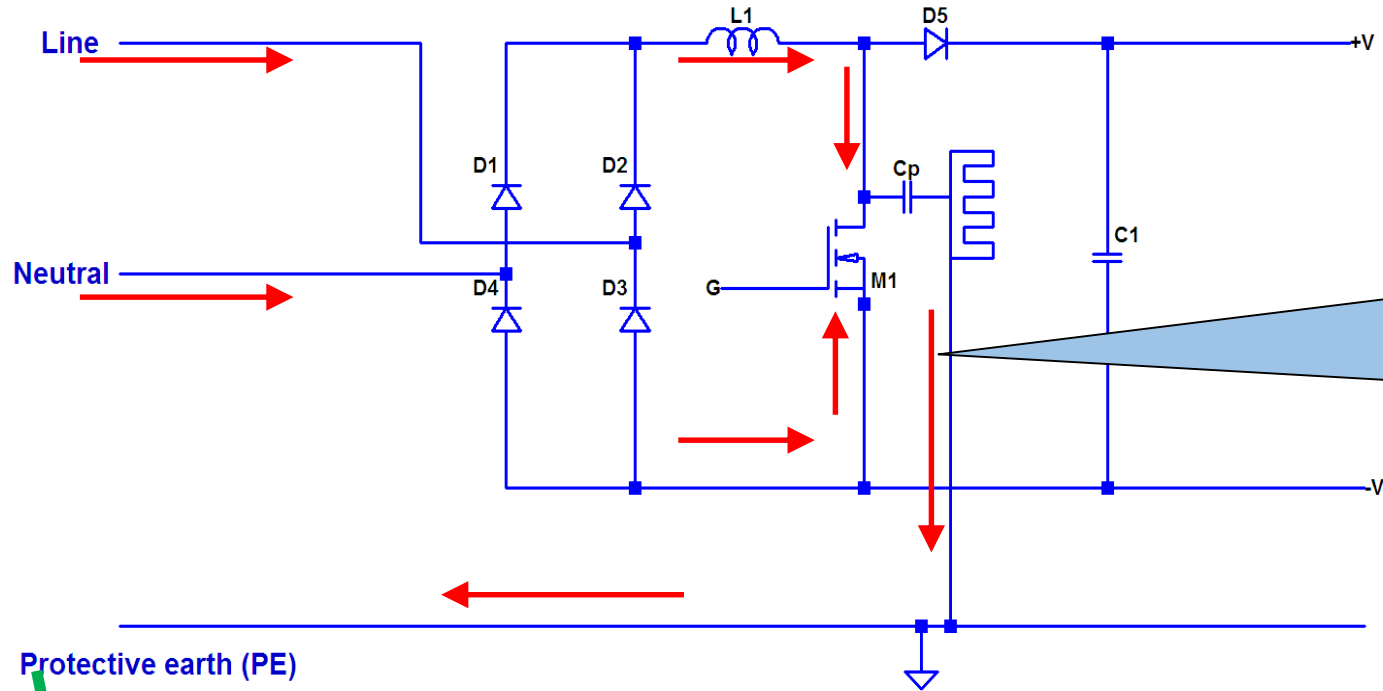

Return current from Cp makes a large loop:
- increases Conducted Emission
- causes self-contamination


Big loops are bad for EMC and should be as small as possible

Reduce loop of the return current

**Reduce loop of the
return current**


How?

Example 1: power factor corrector

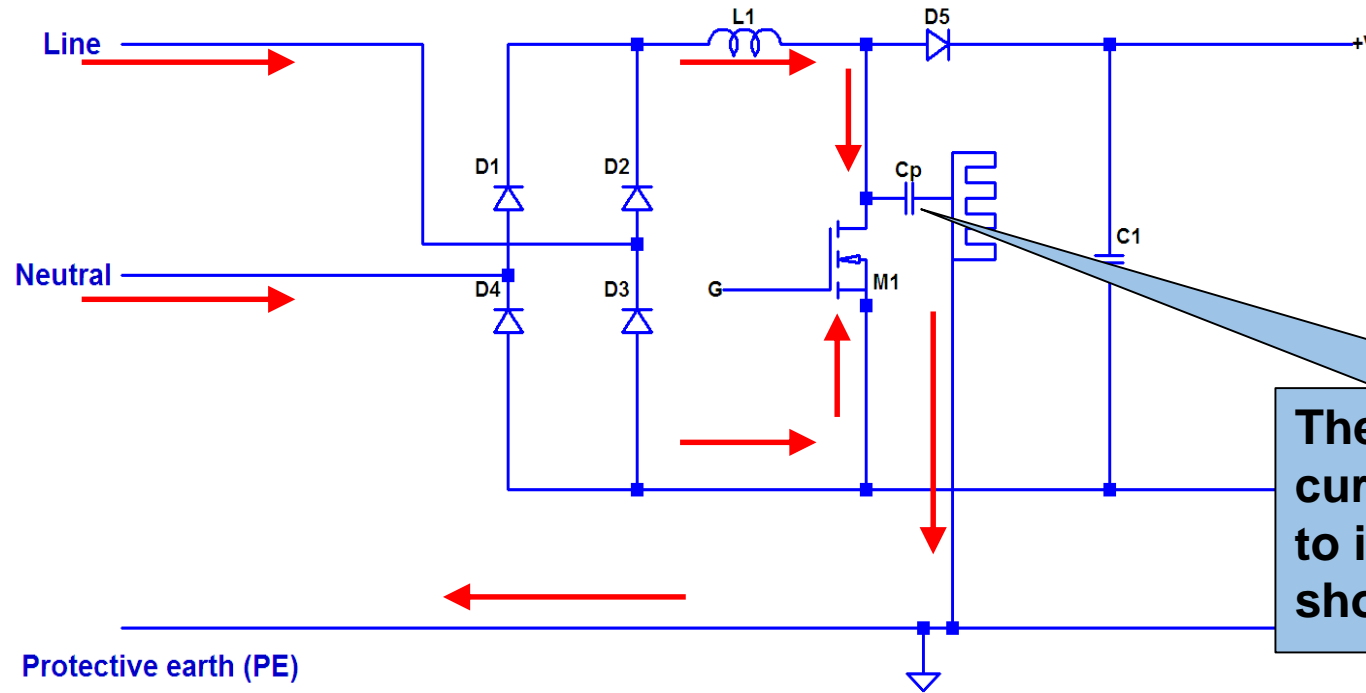

The charge/discharge current of C_p flows back to its origin. This loop should be small.


Example 1: power factor corrector

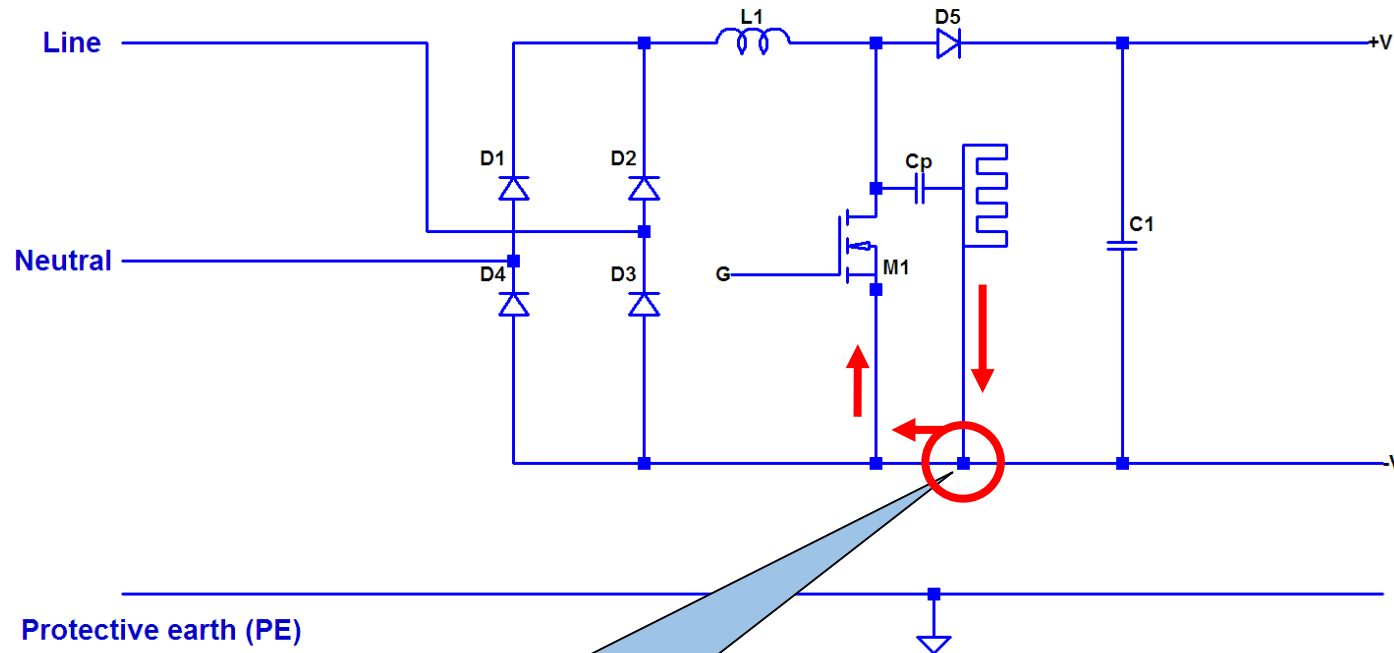


Connect the heat sink to the negative voltage (will have a mechanical impact)

Example 1: power factor corrector

Conducted EMI-measurement:

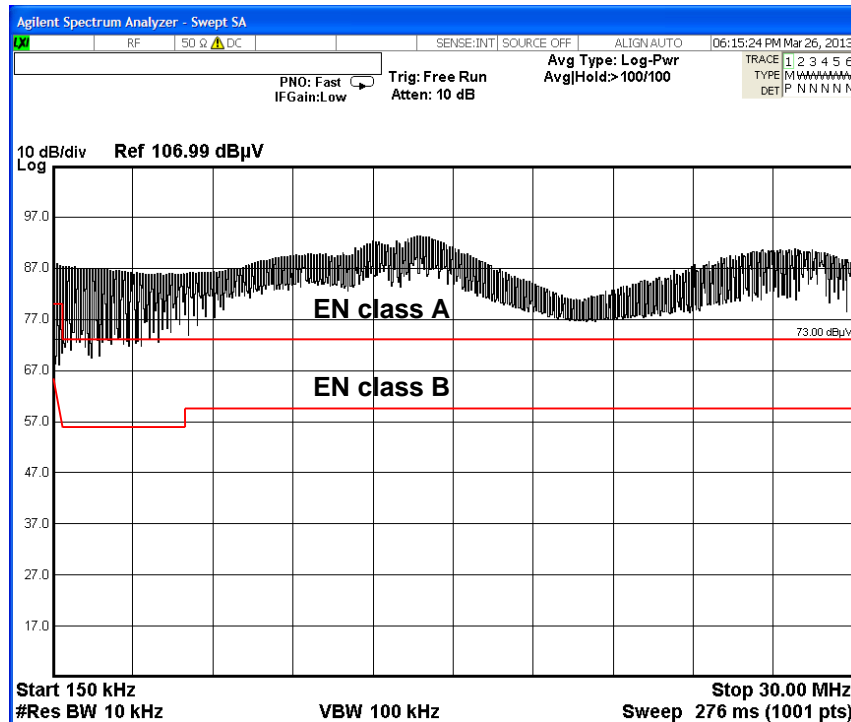


Heat sink to gnd

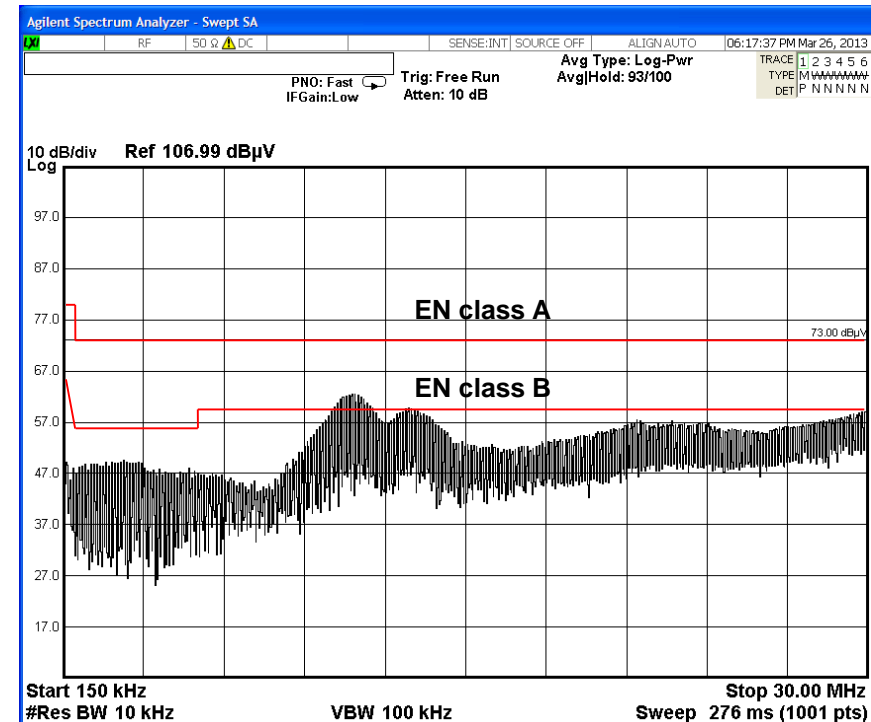


Heat sink to V-


Example 2

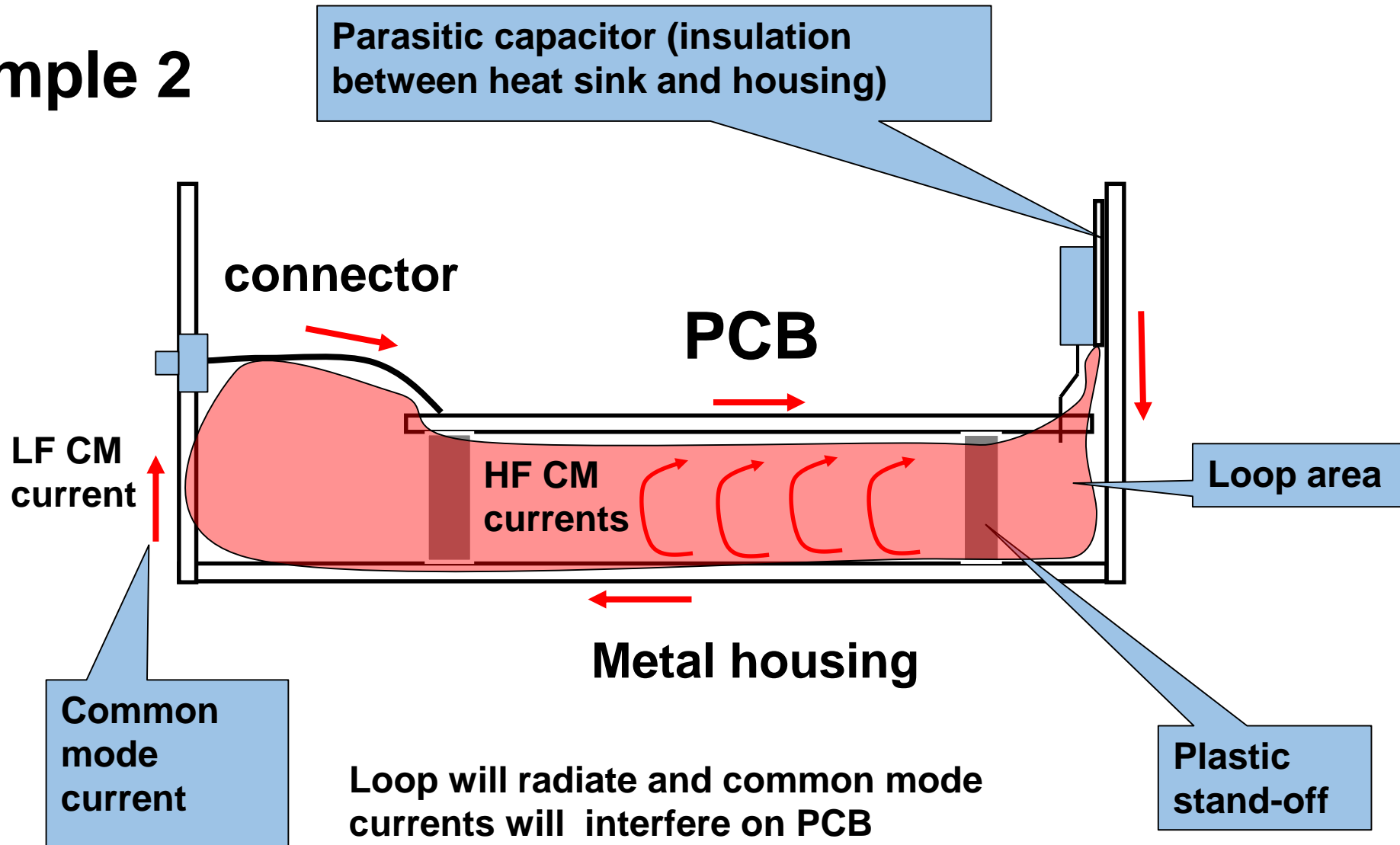


Example 2


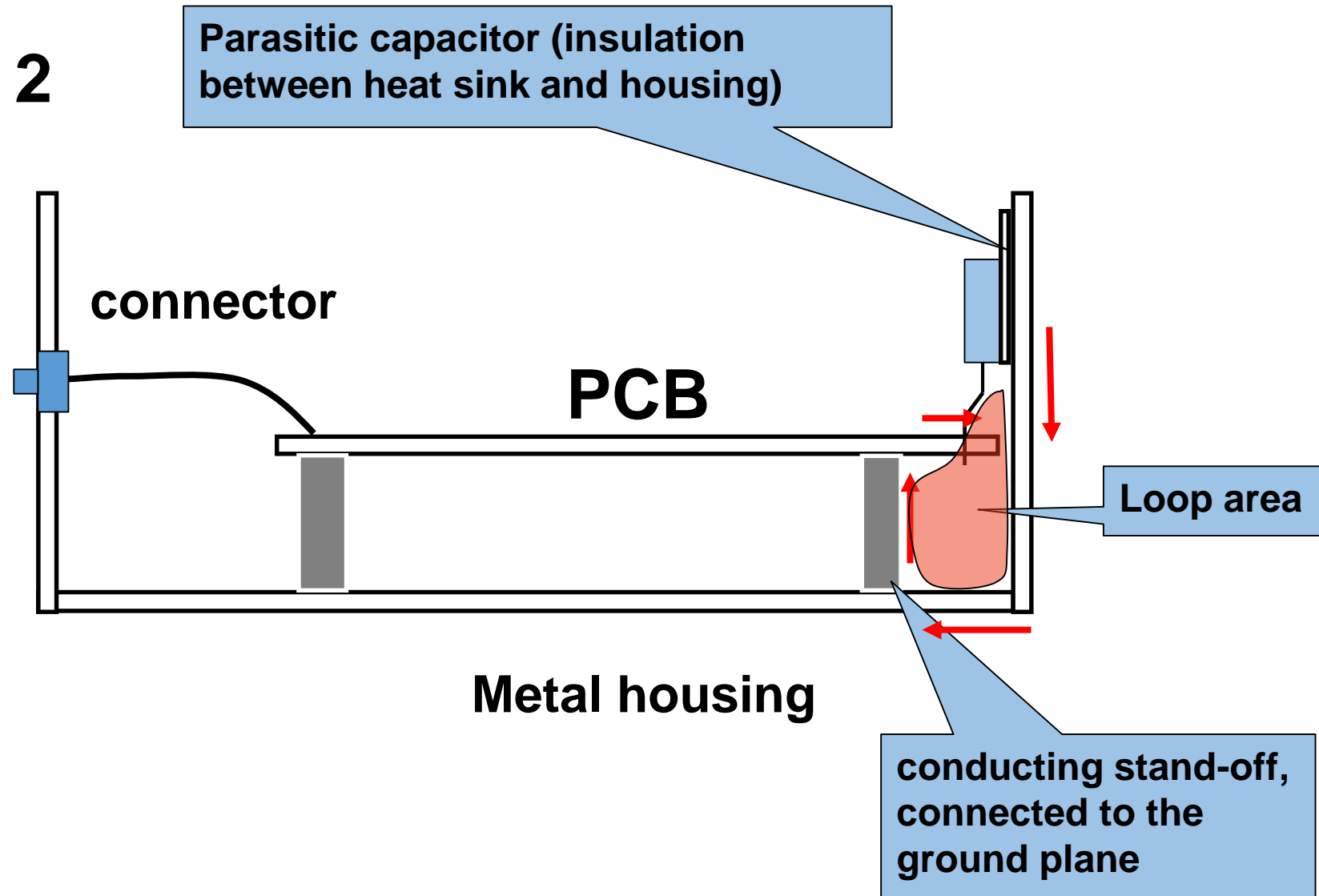


Example 2

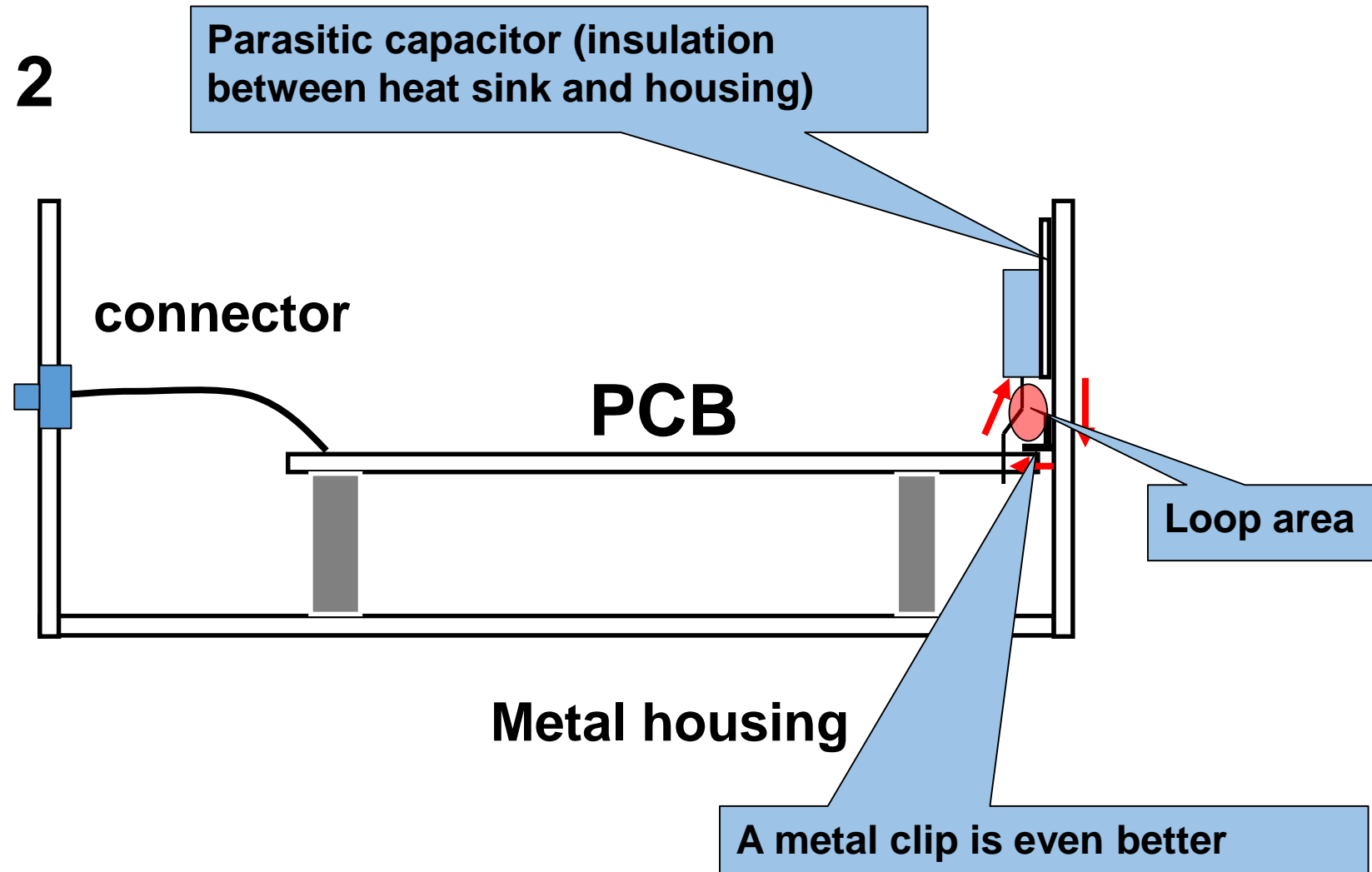


On a larger scale

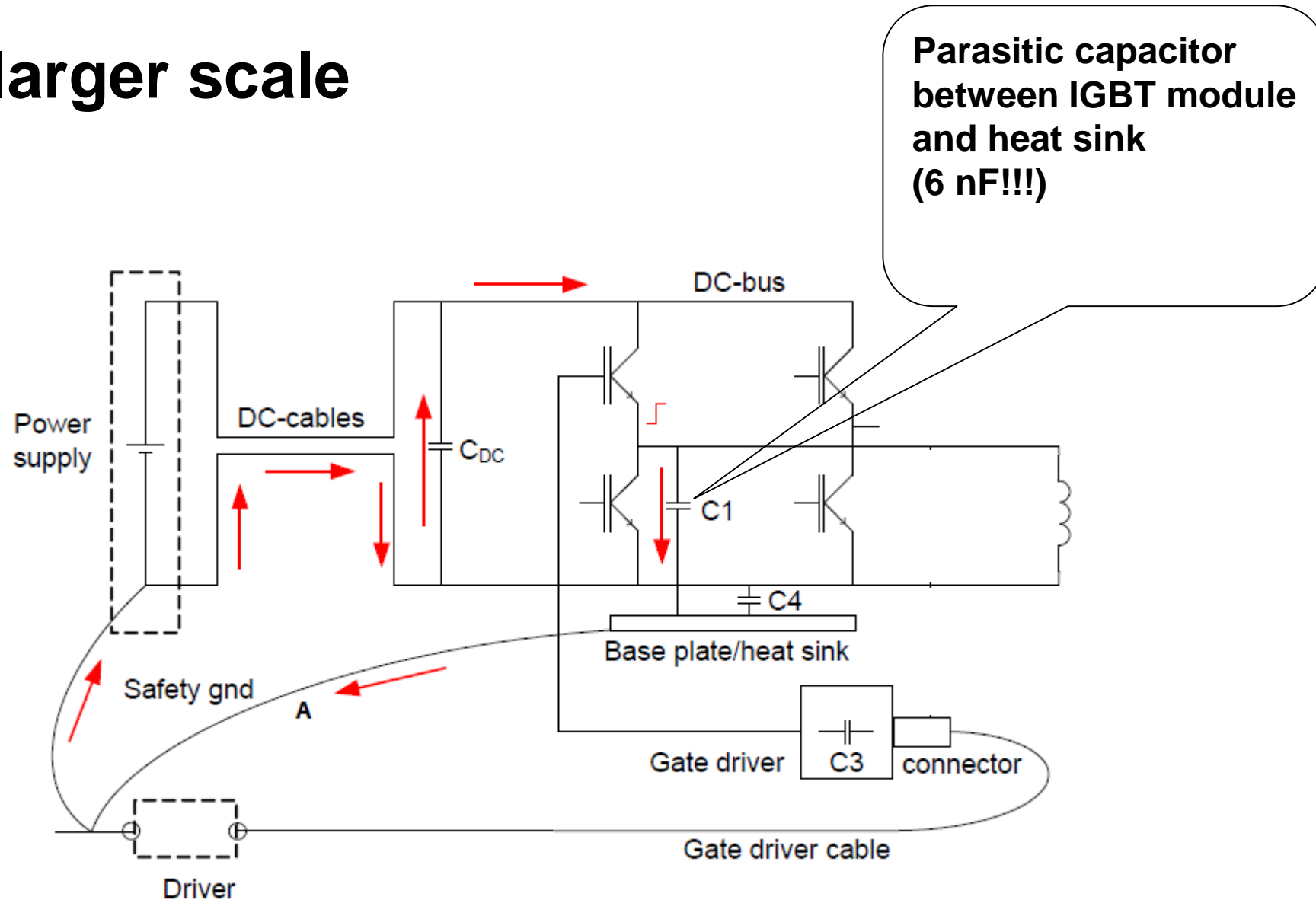

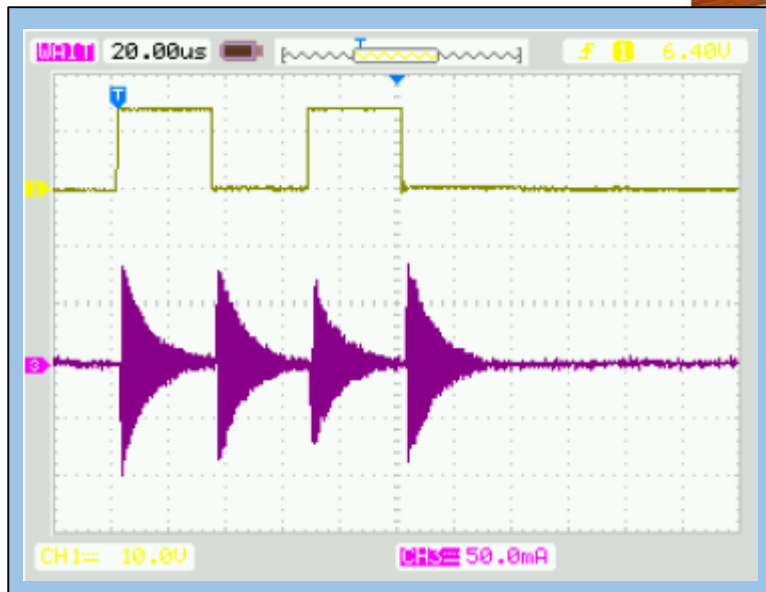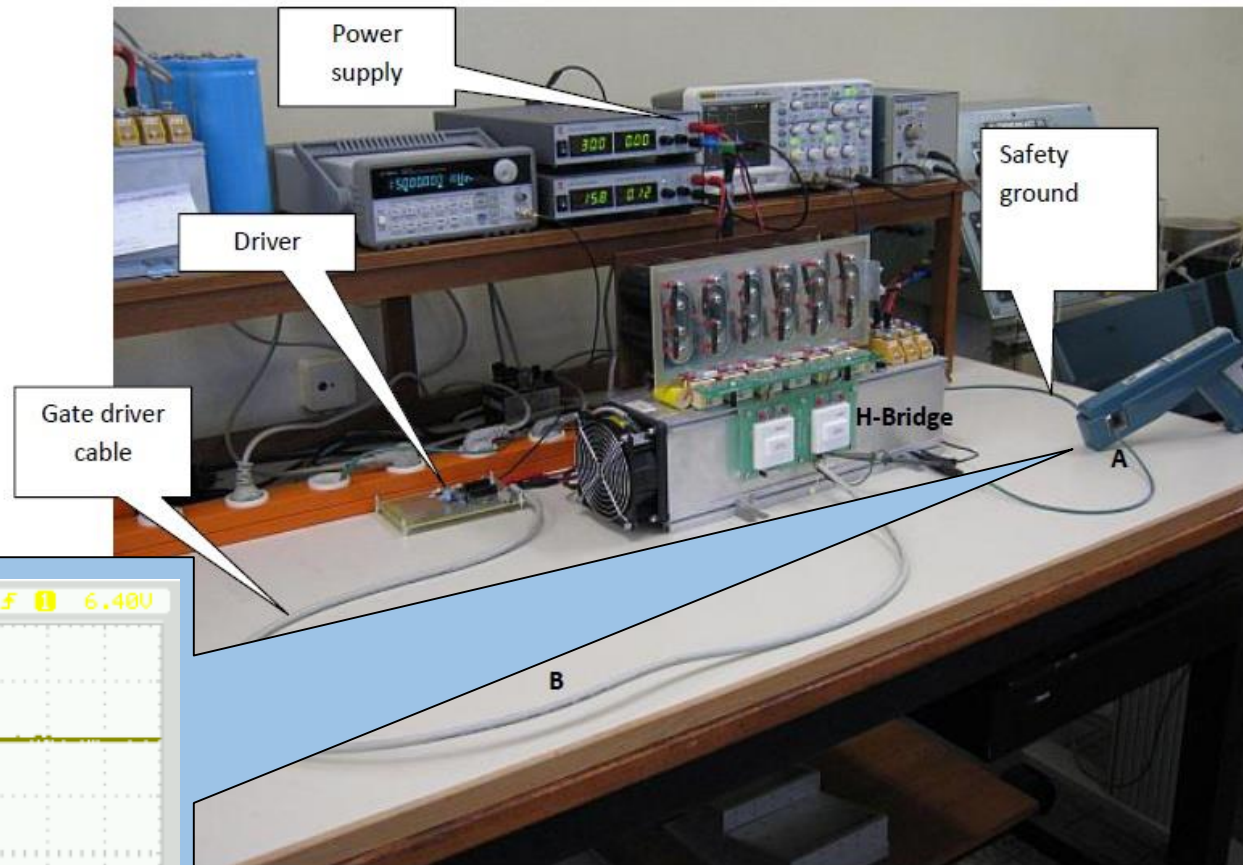


The resonance is caused by the parasitic capacitance and the induction of the return path

Common mode return currents

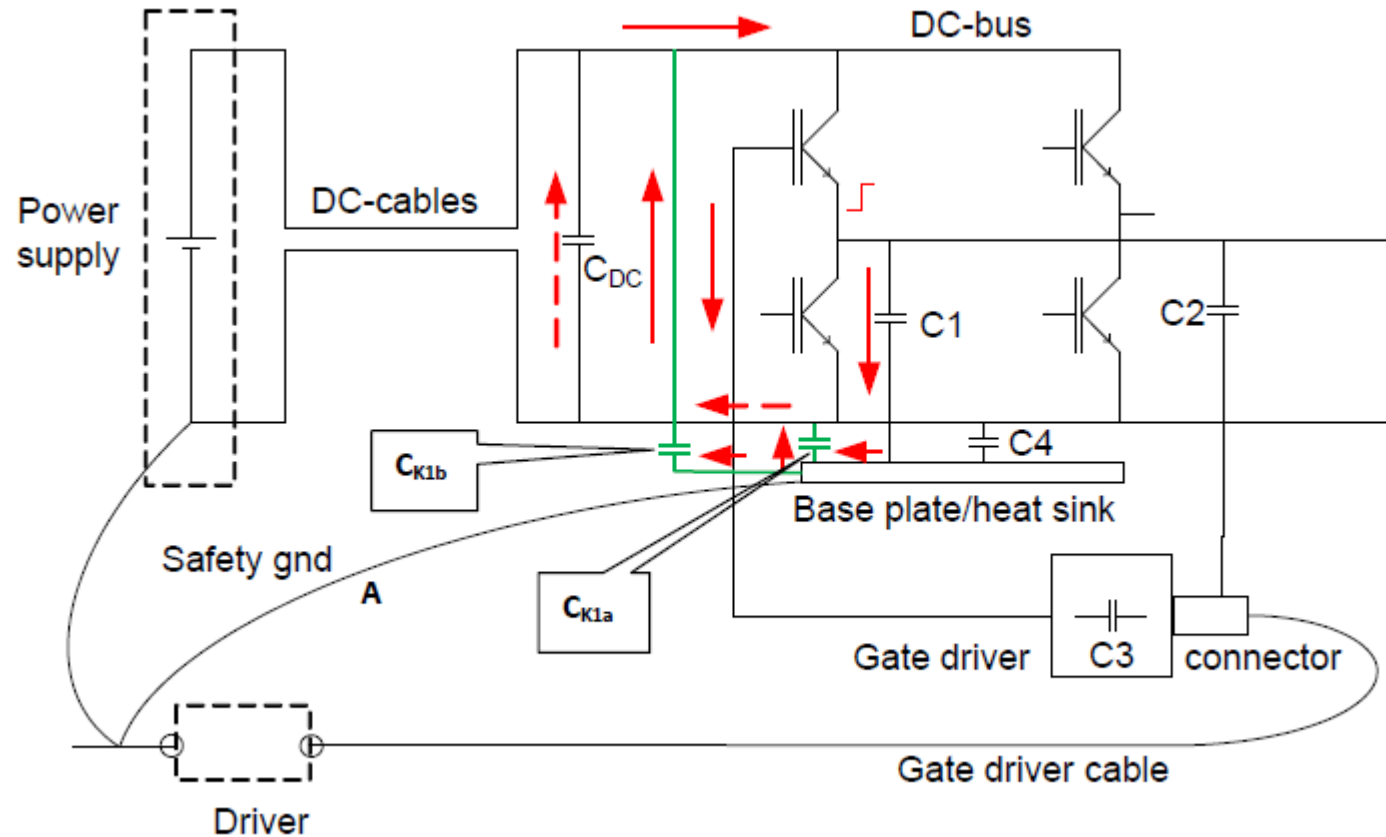

The capacitors are Y-Capacitors

Common mode return currents

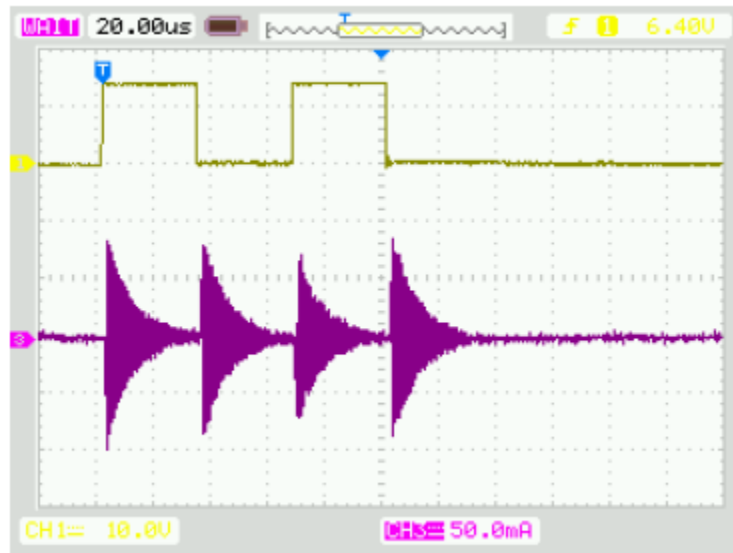


Without Y-capacitors




With Y-capacitors

Common mode return currents

Results differ, depending on the circuit

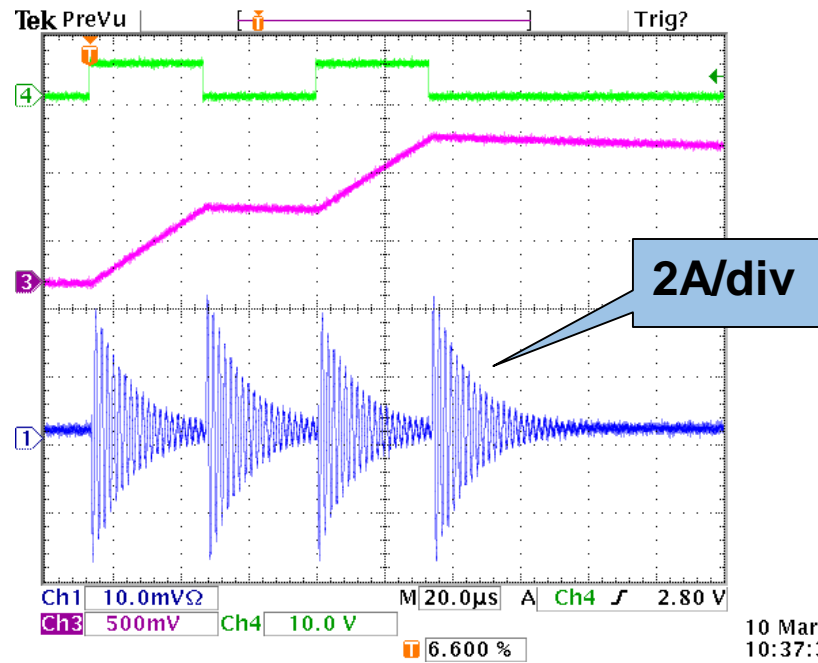

Without Y-capacitors

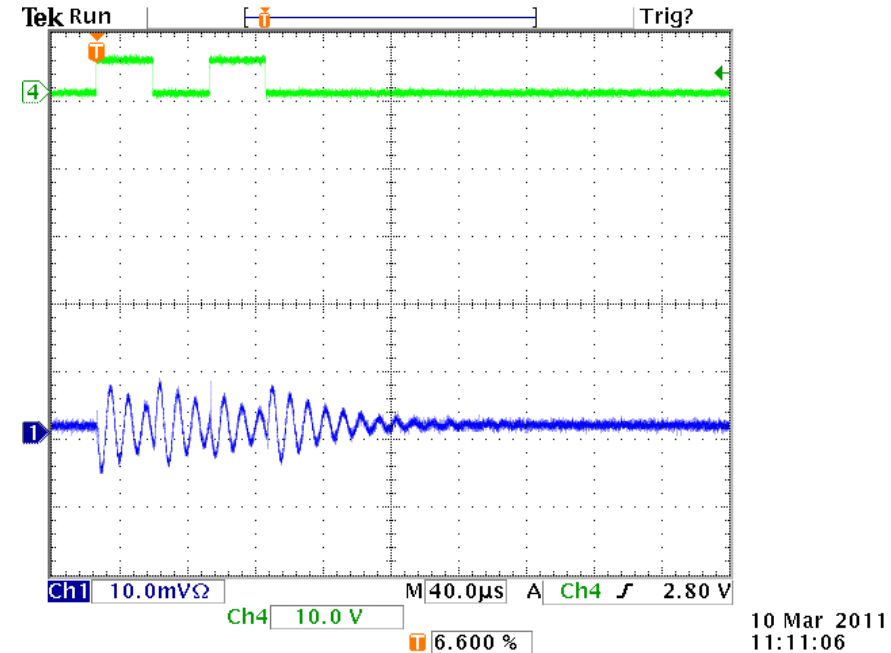

With Y-capacitors

Difference in measured radiation

(Not related to CM)



Without Y-capacitors



With Y-capacitors


Common mode return path

- **Visualize the parasitic capacitor between switching component and cooling surface**
- **Analyze the path of its charge/discharge current**
- **Reduce its loop**


Reducing loops always works

Buck converter on PCB



Manufacturer's reference design

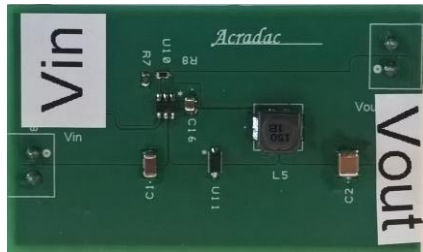

Proper layout with reduced loops

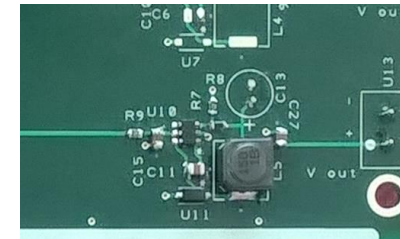

Radiated emission

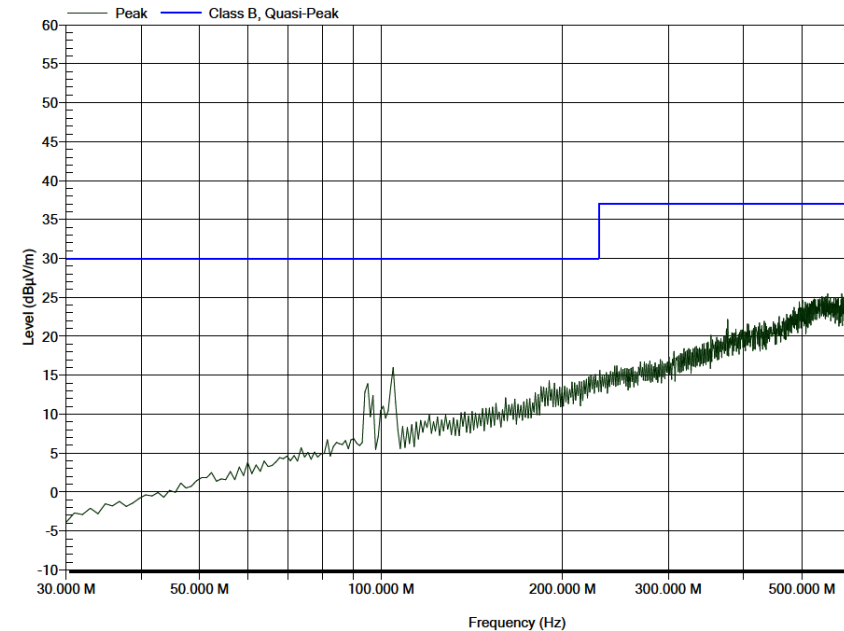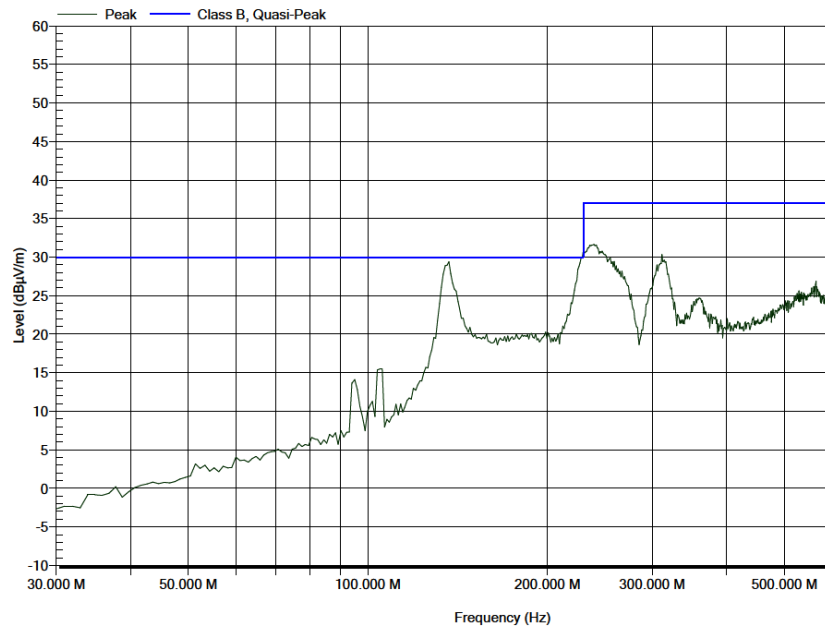

Analyzing the return currents and reducing their loops can easily decrease EMI with 20-25 dB without the need for filters, ferrite beads or shielding

Want to know more?

- **Courses are available from:**

Acradac

EMC Training and Consultancy

www.acradac.com

or visit the stand