



Multilevel Modular Converters (MMC)


E. (Minos) Kontos, MSc.

Contact: e.kontos@tudelft.nl

Outline

- Introduction
- HVDC Stations
- Need for MMC
- Current Practice
- MMC Design Choices
- MMC Basics
- Control Structure
- Challenges in HVDC Grids
- System Integration
- Fault Response

Introduction

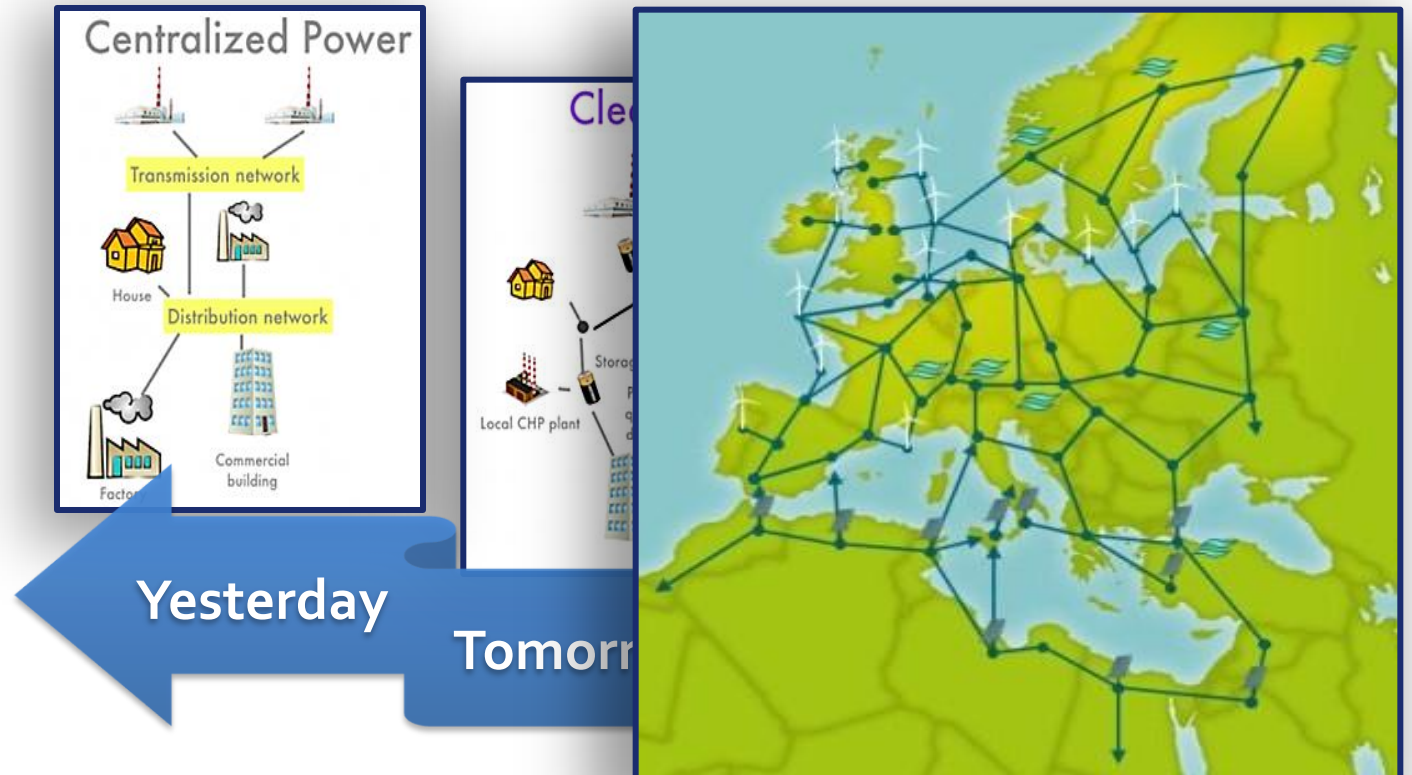

Adapted from: <http://www.ilsr.org>

Source: Friends of Supergrid


HVDC Stations

HVDC Classic



Source: ABB

VSC-HVDC

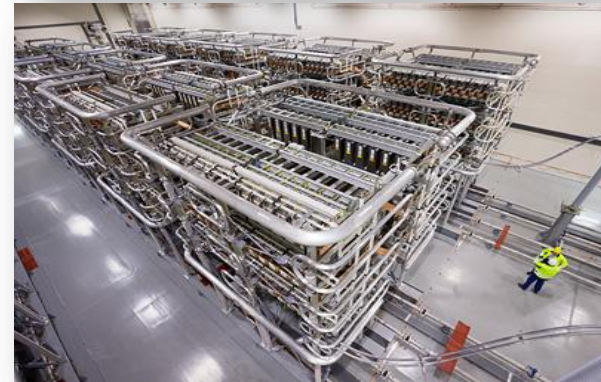

Source: Siemens

Need for Multilevel Converters

- Two-level and diode-clamped topologies are suitable for medium voltage.
- But:
 - Redundancy difficult to achieve.
 - Scale poorly to many levels.
 - Trade-off between switching losses and harmonic performance becomes critical for MV and HV converters.

Multilevel converters are needed!

Current Practice

MMC-HVDC

Offshore wind-power plant (OWPP) connection projects

Project	Capacity (MW)	DC-link Voltage (kV)	Supplier
Borwin Beta	800	± 300	Siemens
Borwin Gamma	900	± 320	Siemens
Dolwin Alpha	800	± 320	ABB
Dolwin Beta	916	± 320	ABB
Dolwin Gamma	900	± 320	GE
Helwin Alpha	576	± 250	Siemens
Helwin Beta	690	± 320	Siemens
Sylwin Alpha	864	± 320	Siemens


Current Practice

MMC-HVDC

Interconnectors


Project	Capacity (MW)	DC-link Voltage (kV)	Supplier
Trans Bay Cable	400	± 200	Siemens
INELFE	2000	± 320	Siemens
NordBalt	700	± 300	ABB
Skaggerrak 4	700	500	ABB
SydVästlänken	2 x 600	± 300	GE
COBRACable	700	± 320	Siemens
ElecLink	1000	± 320	-
Nemo Link	1000	400	Siemens
Viking Link	1400	-	-

MMC design choices

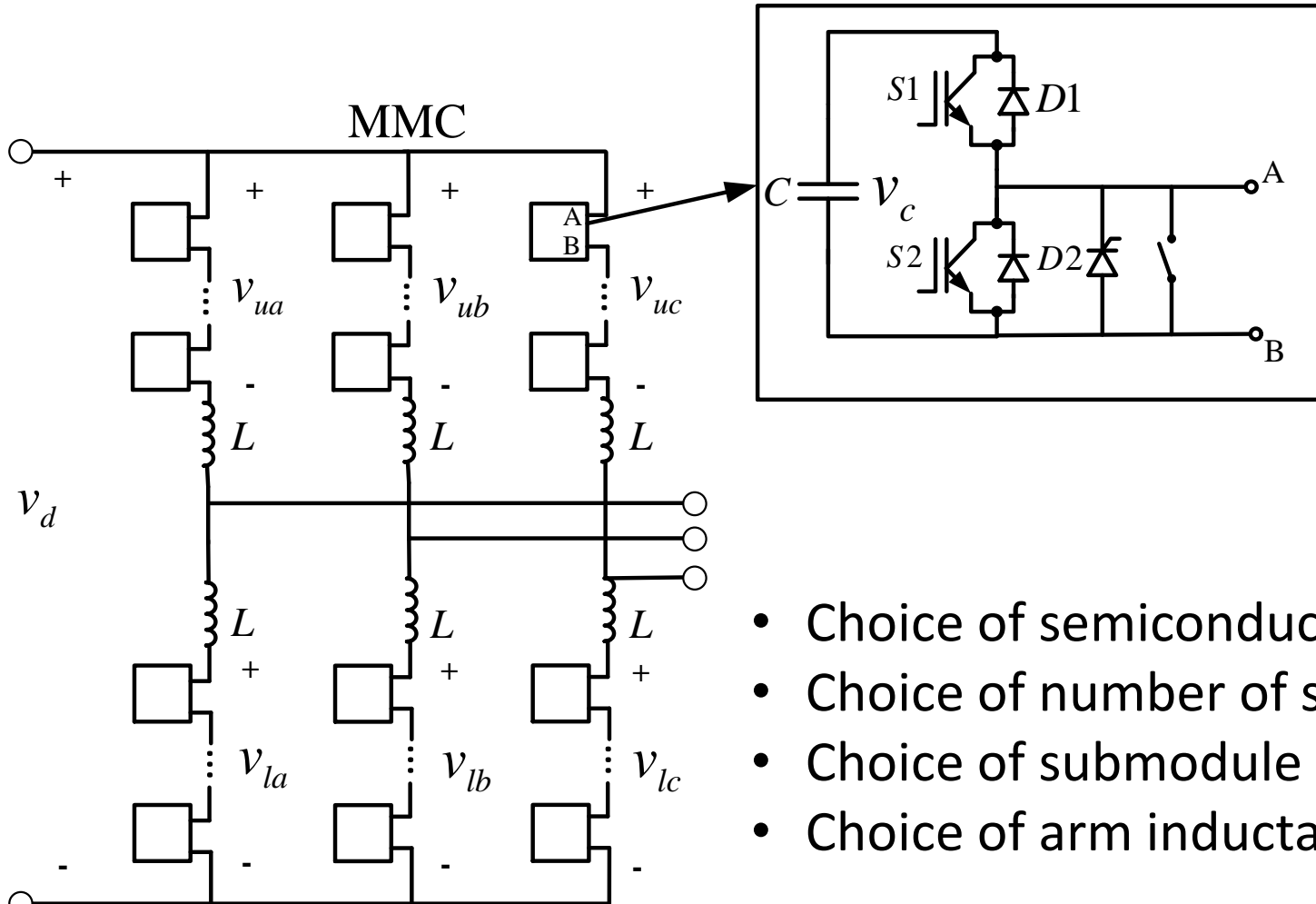

- Choice of semiconductor devices
- Choice of number of submodules (N)
- Choice of submodule capacitance (C)
- Choice of arm inductance (L)

MMC Basics

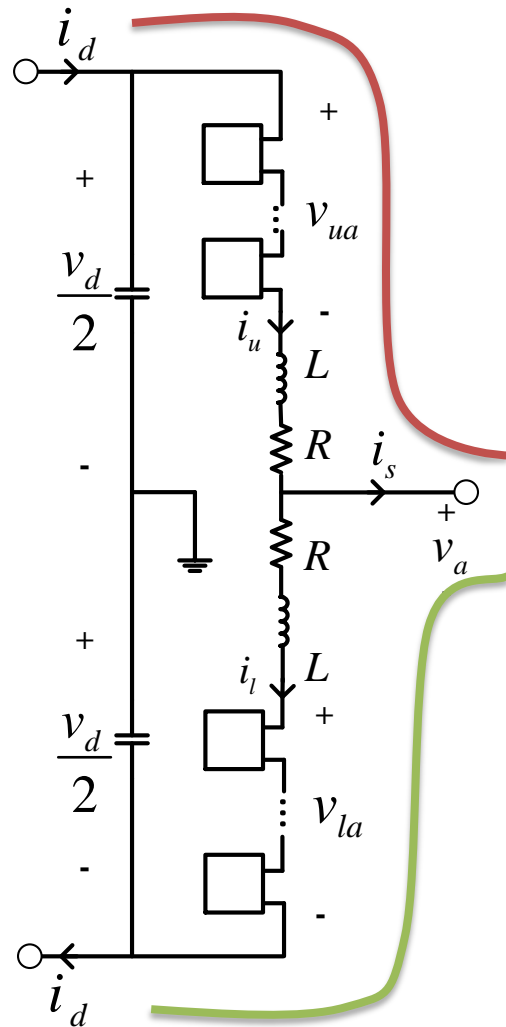

Apply KVL to arm circuits

$$\frac{v_d}{2} = Ri_u + L \frac{di_u}{dt} + v_u + v_a$$

$$\frac{v_d}{2} = Ri_l + L \frac{di_l}{dt} + v_l - v_a$$


From Figure, it is evident that:

$$i_s = i_u - i_l$$


We define the circulating current i_c as:

$$i_c = \frac{i_u + i_l}{2}$$

MMC Equivalent Circuits

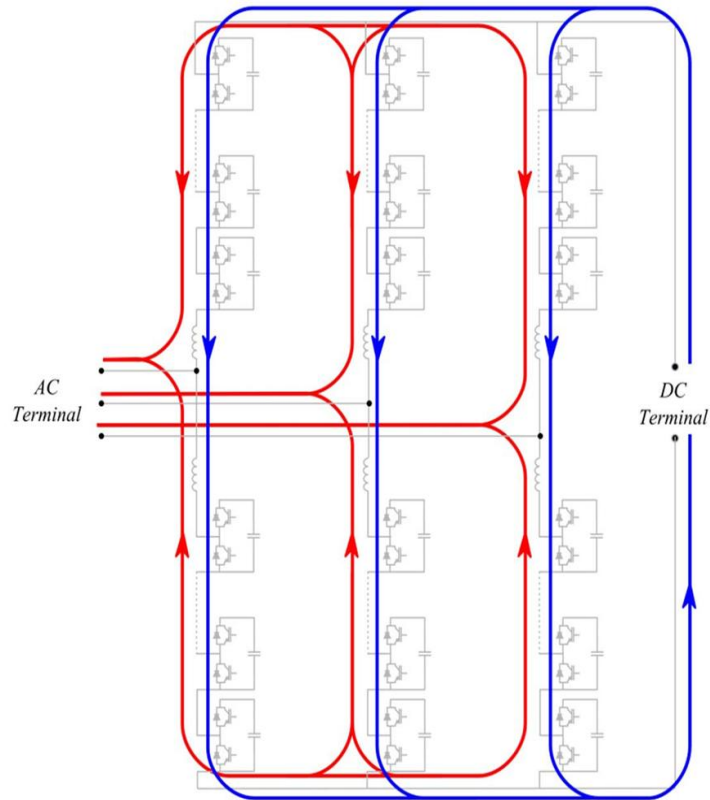

— AC current
— DC current

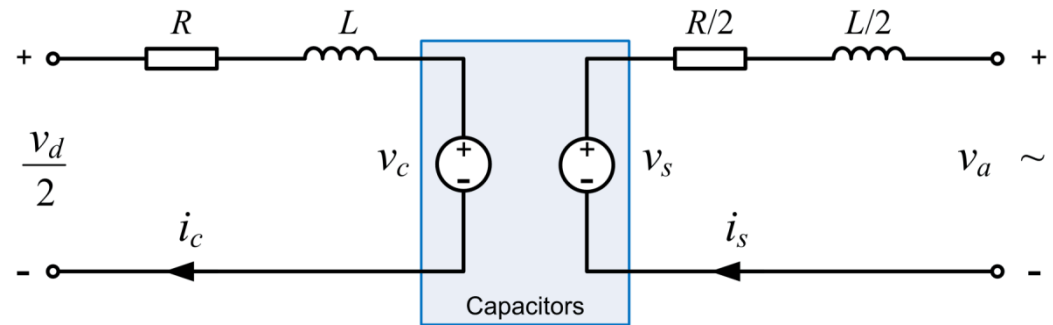

$$\frac{L}{2} \frac{di_s}{dt} = \underbrace{\frac{v_l - v_u}{2}}_{v_s} - v_a - \frac{R}{2} i_s$$

$$L \frac{di_c}{dt} = \frac{v_d}{2} - \underbrace{\frac{v_u + v_l}{2}}_{v_c} - R i_c$$

The output voltage v_s drives the output current i_s .
The internal voltage v_c drives the circulating current i_c .

Insertion Indices


What is insertion index?

Per arm the insertion indices can be calculated as:

$$n_{u,l} = \frac{1}{N} \sum_{i=1}^N n_{u,l}^i$$

This results in the continuous model:

$$v_{u,l} = n_{u,l} v_{cu,l}^{\Sigma}$$

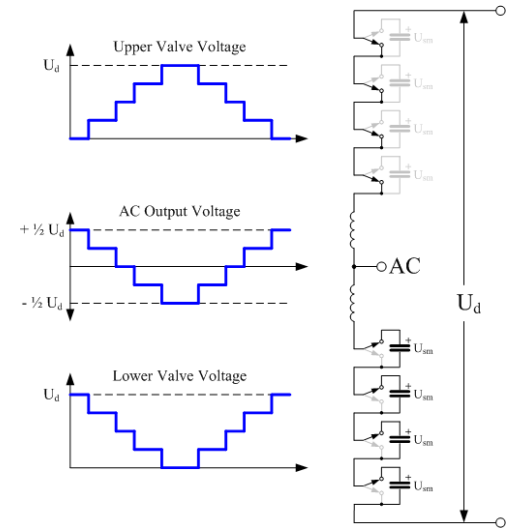

*MMC animation – wikipedia.


So when substituted in the MMC model it yields:

$$L \frac{di_c}{dt} = \frac{v_d}{2} - \frac{n_u v_{cu}^{\Sigma} + n_l v_{cl}^{\Sigma}}{2} - R i_c \quad L \frac{di_s}{dt} = \frac{n_l v_{cl}^{\Sigma} - n_u v_{cu}^{\Sigma}}{2} - v_a - \frac{R}{2} i_s$$

$$\Rightarrow \boxed{n_u = \frac{v_c^* - v_s^*}{v_{cu}^{\Sigma}} \quad n_l = \frac{v_c^* + v_s^*}{v_{cl}^{\Sigma}}}$$

The currents can be controlled via the insertion indices.
The controller has two degrees of freedom.

Control Structure

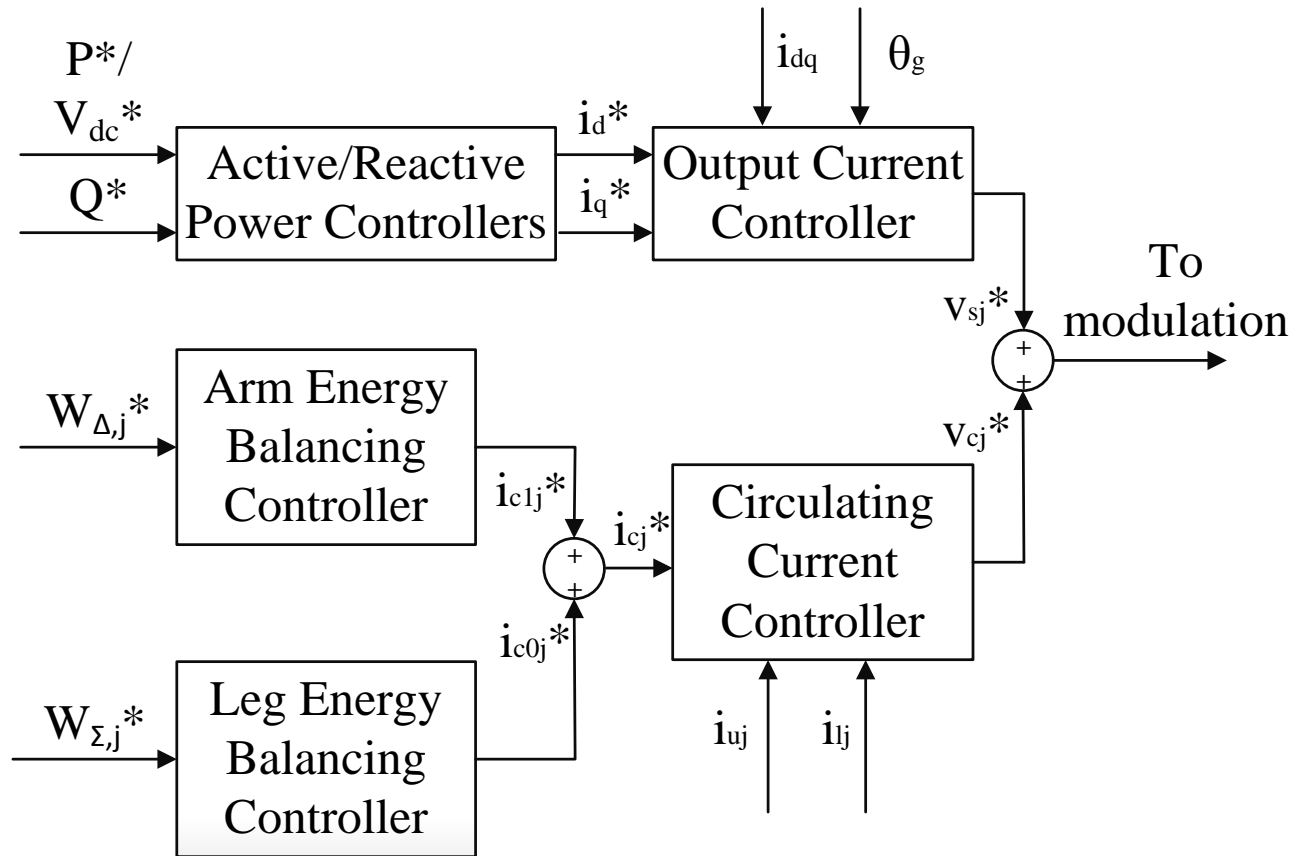

Challenges in HVDC Grids

HVDC grid realization key aspects

System
Integration

Dynamic
Behavior

Fault Response

System Integration

MMC Scalability

- **Massive series connection** of semiconductors is **not required** (as in 2-level VSC) to handle the dc voltage in HV applications;
- **Easily scalable** through plug-in modules (capability of integrating different number of racks in the system);
- **Redundancy**;
- **Optimization** is needed to decide number of SMs vs. levels of harmonic distortion and converter losses.



System Integration

MMC-HVDC Station Components

- **Transformer**
 - **Normal operation:** parallel connection of two transformers at 70-75% of nominal rating, naturally cooled;
 - **Emergency operation:** one transformer, overloaded with possibly forced cooling, which equates to 100% of nominal scheme rating.
- **Phase reactors and DC pole reactors**
 - **Air core phase reactors**
 - Suppress circulating current;
 - Limit rate of rise of fault currents;
 - Located in a separate room next to converter valve hall.

System Integration

MMC-HVDC Station Components

- DC pole reactors
 - In series with converter pole;
 - Smooth dc ripple and harmonics;
 - Limit peak and rate of rise of dc fault currents.
- **Converter valve hall**
 - Two valve halls usually, each containing three arms;
 - Surge arresters on each arm;
 - Each arm has SM stacks;
 - Each SM has IGBTs, dc capacitors, drivers and protection;
 - Forced water-cooling.
- **Additionally:** Control, protection and communication equipment, ac and dc switchyards, auxiliary systems.

System Integration

SIEMENS HVDC PLUS



ABB HVDC Light



GE HVDC MaxSine™




Towards MTdc grids main **challenges** arise:


- Many **different voltage levels** currently used;
- **Lack of HVDC equipment standardization**;
- **Different design approaches** by major manufacturers;
- **Different protection principles**;
- **Different control** structures with limitation in coordination;
- **Communication issues.**

Protection Issues


Half-bridge MMC-HVDC connections

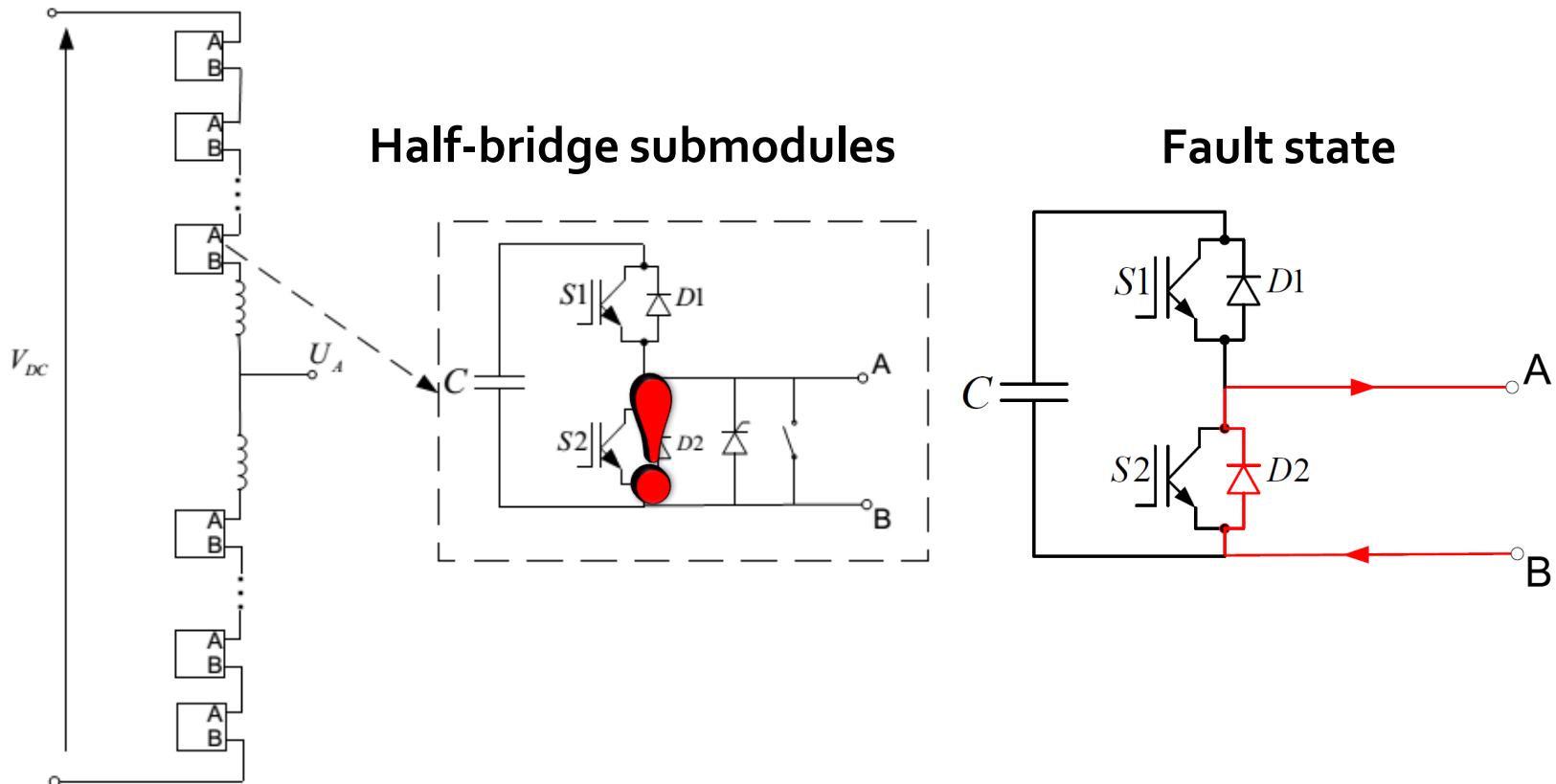

Protection Issues

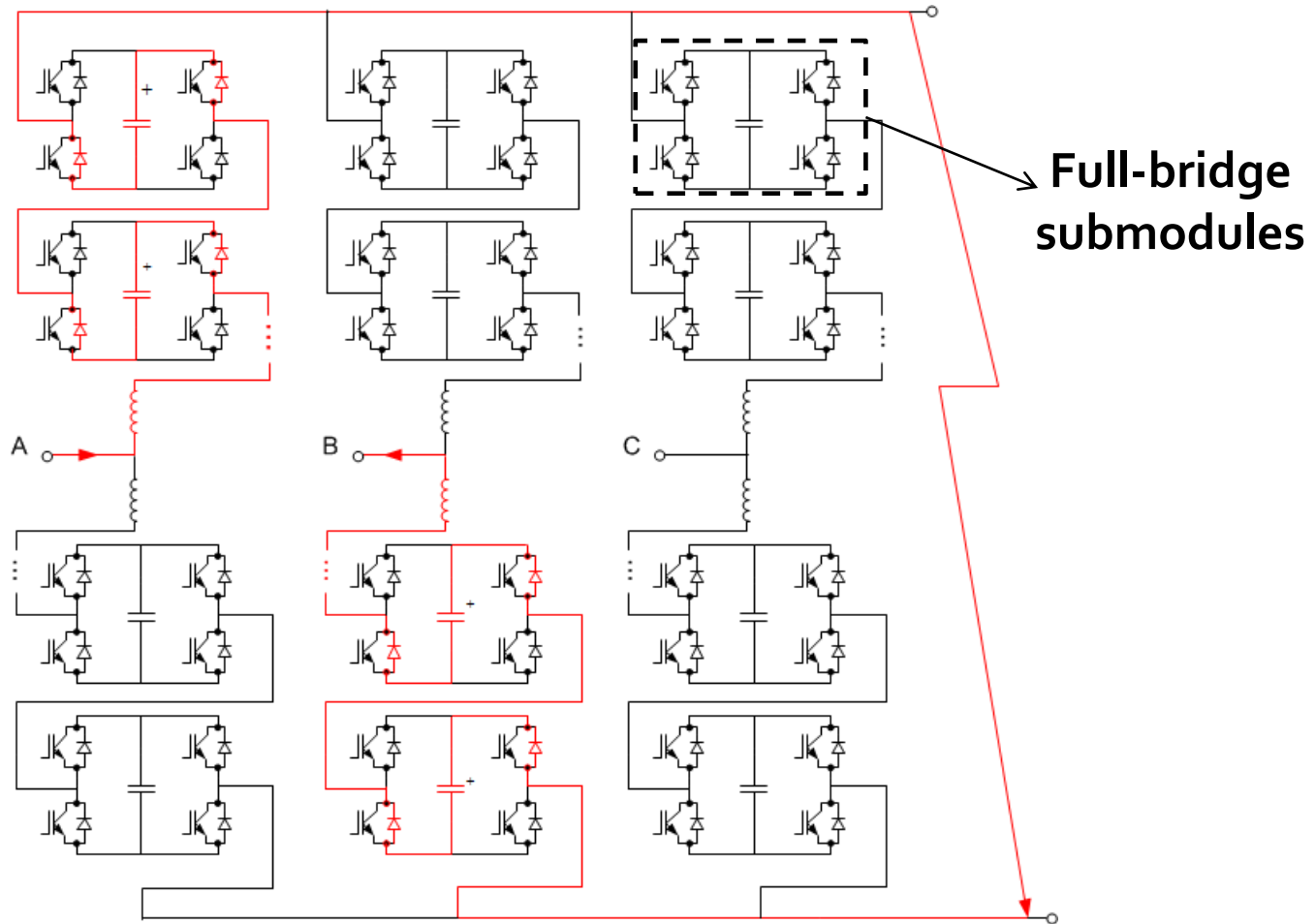

DC Fault Detection

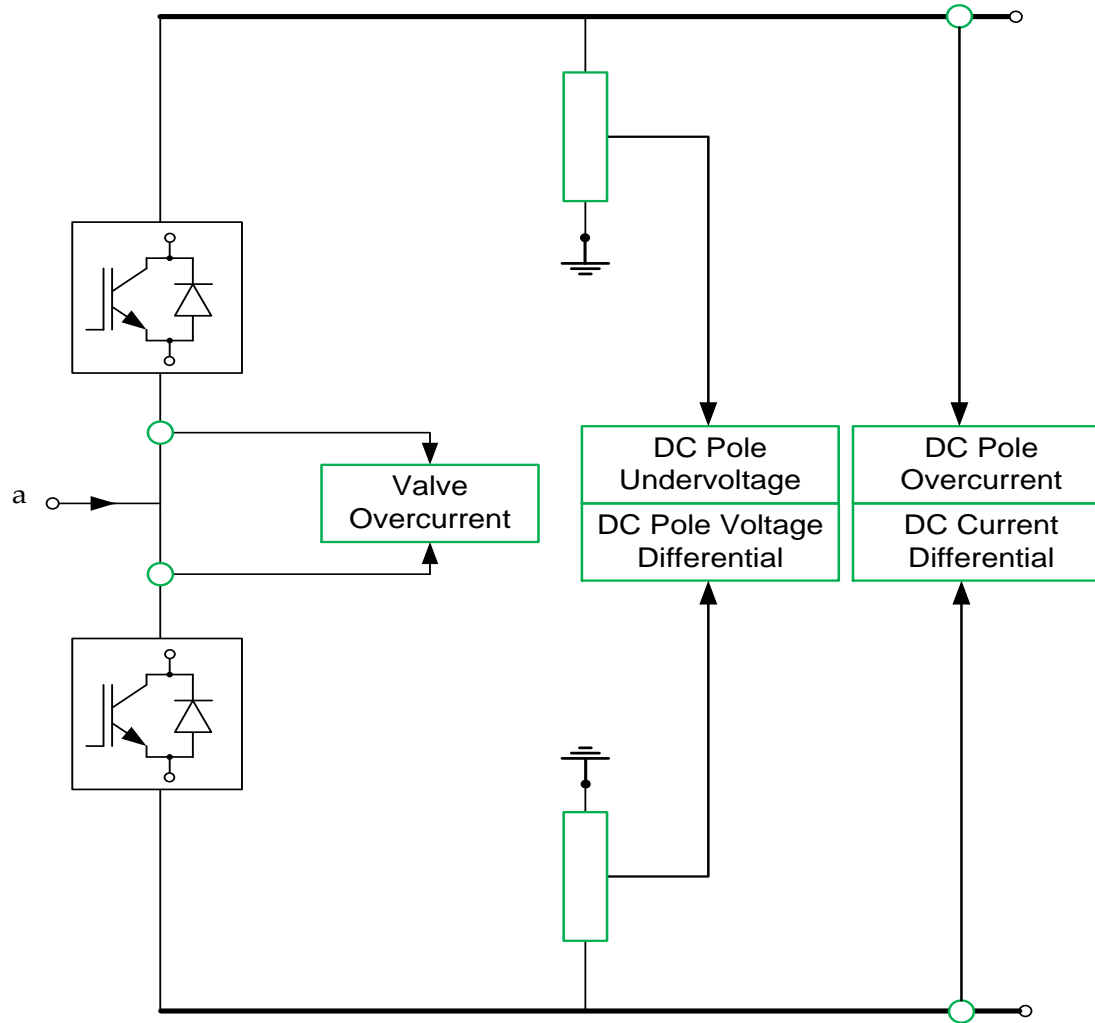

Summary

- Design, control and integration of MMC in a grid is a multifaceted problem.
- System integration studies reveal the advantages of MMC technology.
- MMC provides additional operational flexibility in contingencies both on the ac and the dc side.

Questions?

